

ConcepTest PowerPoints

Chapter 18

Physics: Principles with Applications, 6th edition

Giancoli

© 2005 Pearson Prentice Hall

This work is protected by United States copyright laws and is provided solely for the use of instructors in teaching their courses and assessing student learning. Dissemination or sale of any part of this work (including on the World Wide Web) will destroy the integrity of the work and is not permitted. The work and materials from it should never be made available to students except by instructors using the accompanying text in their classes. All recipients of this work are expected to abide by these restrictions and to honor the intended pedagogical purposes and the needs of other instructors who rely on these materials.


ConceptTest 18.1

Which is the correct way to light the lightbulb with the battery?


Connect the Battery

4) all are correct


5) none are correct

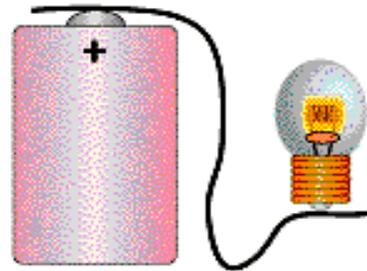

1)

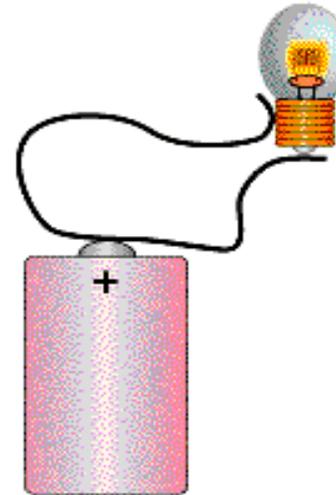

2)

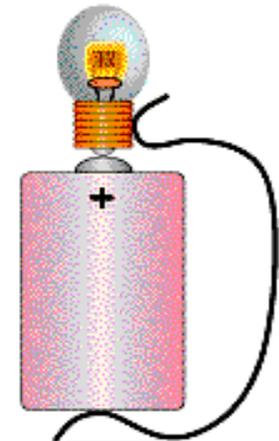

3)



ConceptTest 18.1

Connect the Battery

Which is the correct way to light the lightbulb with the battery?

4) all are correct

5) none are correct

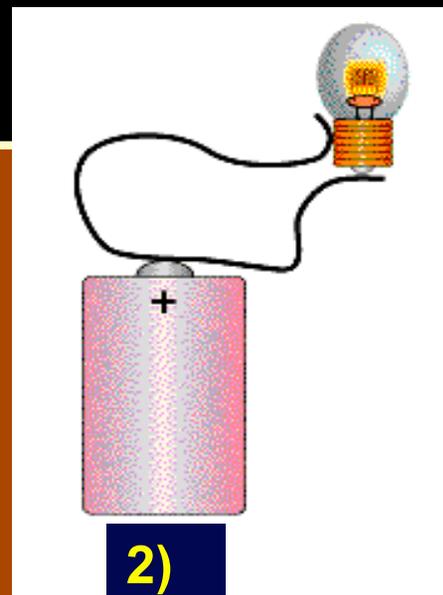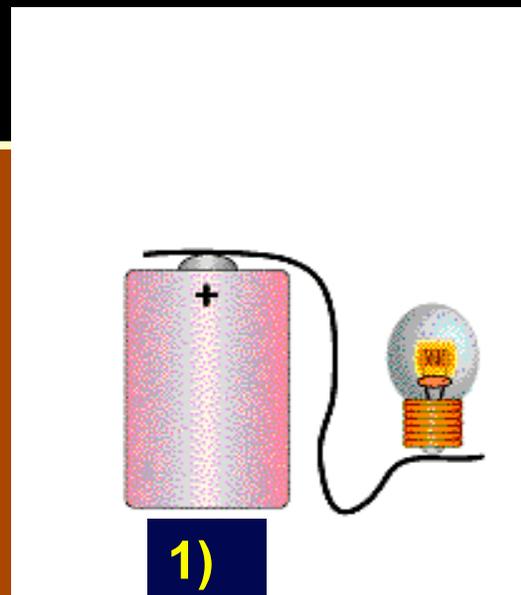

Current can only flow if there is a **continuous connection** from the negative terminal through the bulb to the positive terminal. This is only the case for Fig. (3).

ConceptTest 18.2

Ohm's Law

You double the **voltage** across a certain conductor and you observe the **current** increases three times. What can you conclude?

- 1) Ohm's law is obeyed since the current still increases when V increases
- 2) Ohm's law is not obeyed
- 3) This has nothing to do with Ohm's law



ConceptTest 18.2

Ohm's Law

You double the **voltage** across a certain conductor and you observe the **current** increases three times. What can you conclude?

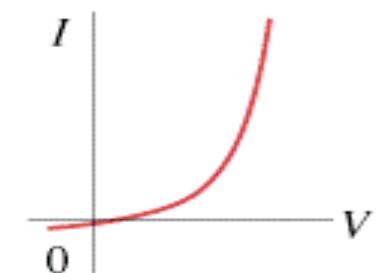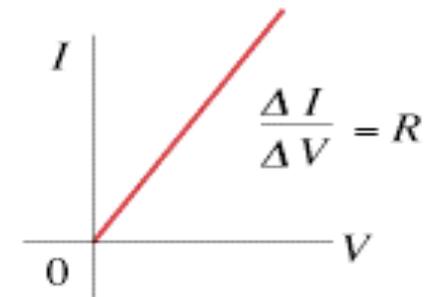- 1) Ohm's law is obeyed since the current still increases when V increases
- 2) Ohm's law is not obeyed
- 3) This has nothing to do with Ohm's law

Ohm's law, $V = IR$, states that the relationship between voltage and current is **linear**. Thus for a conductor that obeys Ohm's Law, the current must double when you double the voltage.



Follow-up: Where could this situation occur?

ConceptTest 18.3a

Wires I

Two wires, **A** and **B**, are made of the same metal and have equal length, but the resistance of wire **A** is four times the resistance of wire **B**. How do their diameters compare?

1) $d_A = 4 d_B$

2) $d_A = 2 d_B$

3) $d_A = d_B$

4) $d_A = 1/2 d_B$

5) $d_A = 1/4 d_B$

ConceptTest 18.3a

Wires I

Two wires, **A** and **B**, are made of the same metal and have equal length, but the resistance of wire **A** is four times the resistance of wire **B**. How do their diameters compare?

1) $d_A = 4 d_B$

2) $d_A = 2 d_B$

3) $d_A = d_B$

4) $d_A = 1/2 d_B$

5) $d_A = 1/4 d_B$

The resistance of wire **A** is greater because its area is less than wire **B**. Since area is related to radius (or diameter) squared, the diameter of **A** must be two times less than **B**.

$$R = \rho \frac{L}{A}$$

ConceptTest 18.3b

Wires II

A wire of resistance R is stretched uniformly (keeping its volume constant) until it is twice its original length. What happens to the resistance?

- 1) it decreases by a factor 4
- 2) it decreases by a factor 2
- 3) it stays the same
- 4) it increases by a factor 2
- 5) it increases by a factor 4

ConceptTest 18.3b

Wires II

A wire of resistance R is stretched uniformly (keeping its volume constant) until it is twice its original length. What happens to the resistance?

- 1) it decreases by a factor 4
- 2) it decreases by a factor 2
- 3) it stays the same
- 4) it increases by a factor 2
- 5) it increases by a factor 4

Keeping the volume (= area x length) constant means that if the length is doubled, the area is halved.

Since $R = \rho \frac{L}{A}$, this increases the resistance by four.

ConceptTest 18.4

Dimmer

When you rotate the knob of a light dimmer, what is being changed in the electric circuit?

- 1) the power**
- 2) the current**
- 3) the voltage**
- 4) both (1) and (2)**
- 5) both (2) and (3)**

ConceptTest 18.4

Dimmer

When you rotate the knob of a light dimmer, what is being changed in the electric circuit?

- 1) the power
- 2) the current
- 3) the voltage
- 4) both (1) and (2)
- 5) both (2) and (3)

The voltage is provided at 120 V from the outside. The light dimmer increases the resistance and therefore decreases the current that flows through the lightbulb.


Follow-up: Why does the voltage not change?

ConceptTest 18.5a

Two lightbulbs operate at 120 V, but one has a power rating of **25 W** while the other has a power rating of **100 W**. Which one has the greater resistance?

Lightbulbs

- 1) the 25 W bulb
- 2) the 100 W bulb
- 3) both have the same
- 4) this has nothing to do with resistance

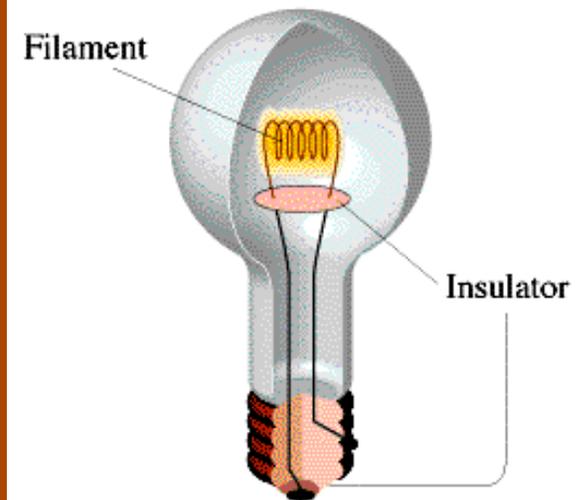


ConceptTest 18.5a

Two lightbulbs operate at 120 V, but one has a power rating of **25 W** while the other has a power rating of **100 W**. Which one has the greater resistance?

Lightbulbs

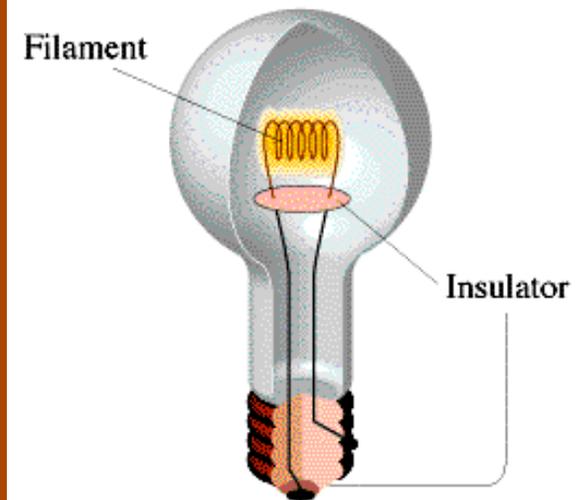- 1) the 25 W bulb
- 2) the 100 W bulb
- 3) both have the same
- 4) this has nothing to do with resistance

Since $P = V^2 / R$ the bulb with the lower power rating has to have the higher resistance.



Follow-up: Which one carries the greater current?

ConceptTest 18.5b

Space Heaters I

Two space heaters in your living room are operated at 120 V.

Heater 1 has **twice** the resistance of heater 2. Which one will give off more heat?

- 1) **heater 1**
- 2) **heater 2**
- 3) **both equally**

ConceptTest 18.5b

Space Heaters I

Two space heaters in your living room are operated at 120 V. Heater 1 has **twice** the resistance of heater 2. Which one will give off more heat?

- 1) heater 1
- 2) heater 2
- 3) both equally

Using $P = V^2 / R$, the heater with the **smaller resistance** will have the **larger power** output. Thus, heater 2 will give off more heat.

Follow-up: Which one carries the greater current?