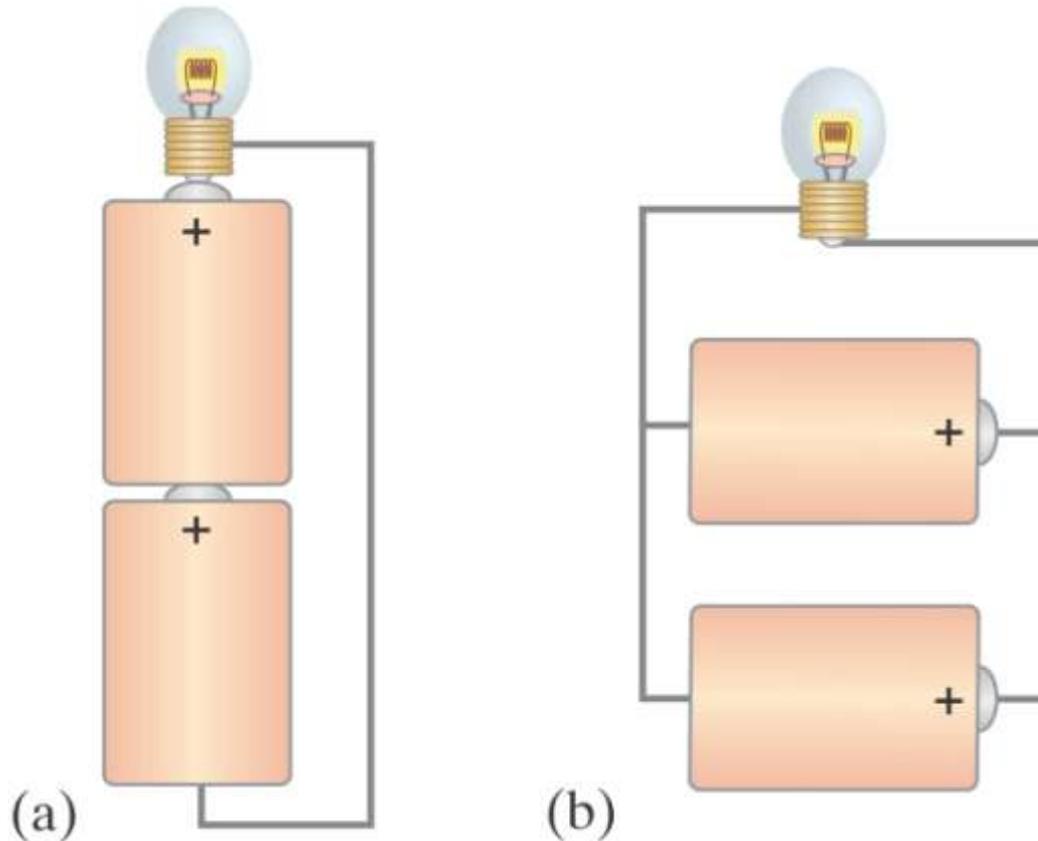


# Chapter 18


## Electric Currents



# 18.1 The Electric Battery

**Volta discovered that electricity could be created if dissimilar metals were connected by a conductive solution called an electrolyte.**

**This is a simple electric cell.**

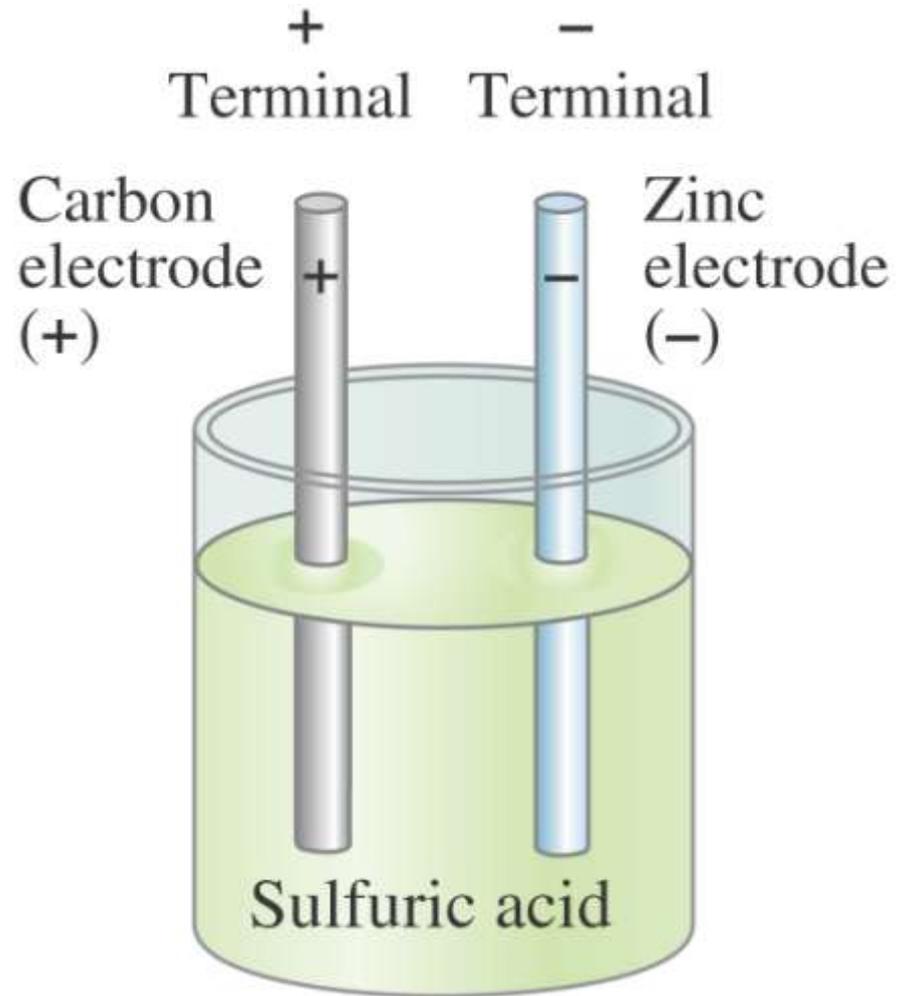


# 18.1 The Electric Battery

**A battery transforms chemical energy into electrical energy.**

**Chemical reactions within the cell create a potential difference between the terminals by slowly dissolving them. This potential difference can be maintained even if a current is kept flowing, until one or the other terminal is completely dissolved.**
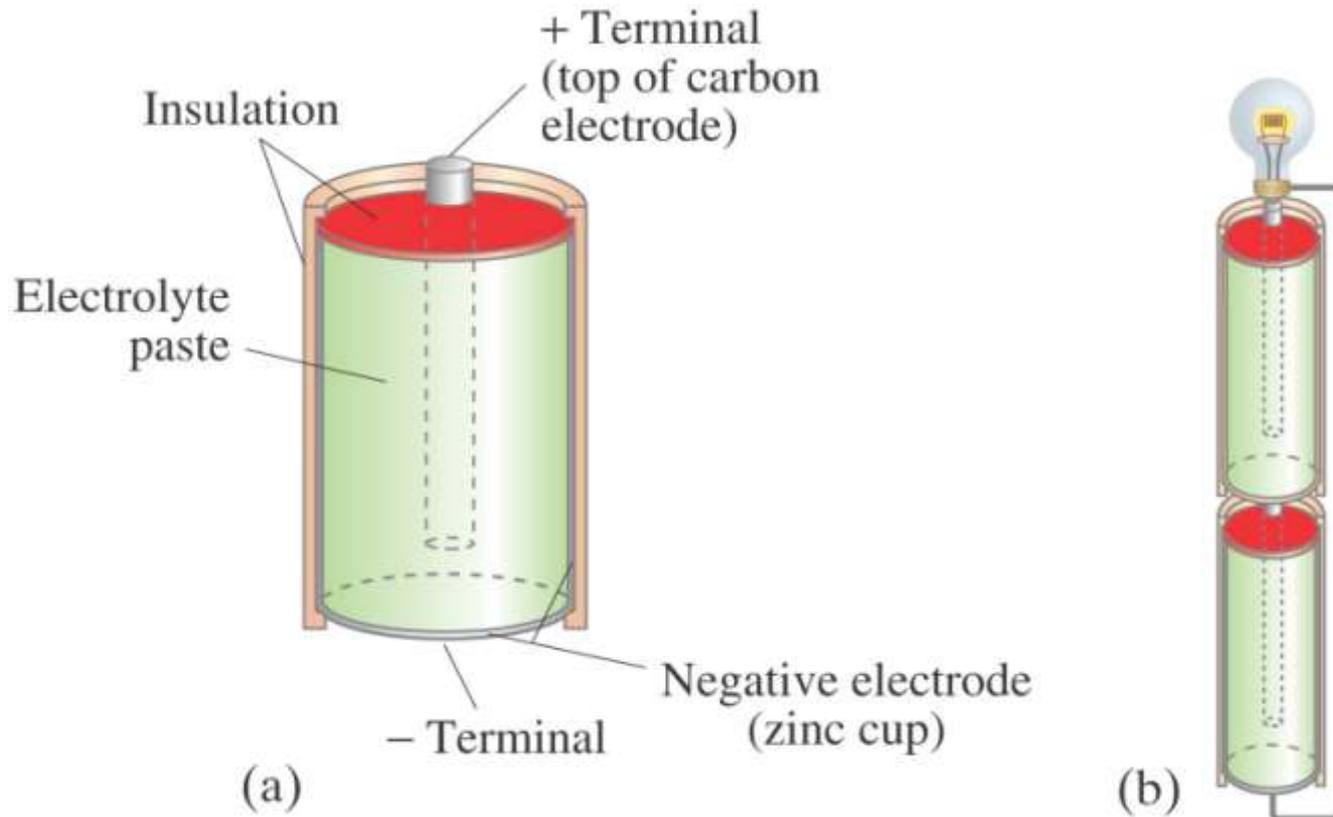
# 18.1 The Electric Battery

Several cells connected together make a battery, although now we refer to a single cell as a battery as well.



## 18.2 Electric Current

**Electric current is the rate of flow of charge through a conductor:**

$$I = \frac{\Delta Q}{\Delta t} \quad (18-1)$$

**Unit of electric current: the ampere, A.**


$$1 \text{ A} = 1 \text{ C/s.}$$

# 18.2 Electric Current

**A complete circuit is one where current can flow all the way around. Note that the schematic drawing doesn't look much like the physical circuit!**




(a)

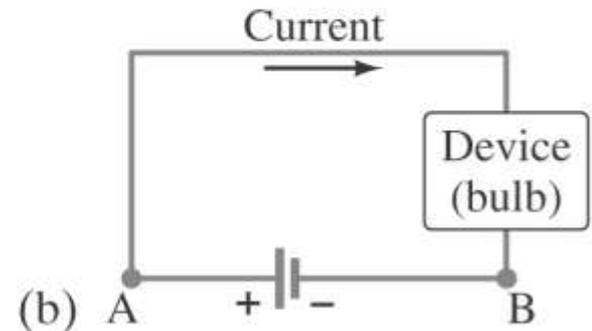

(b)

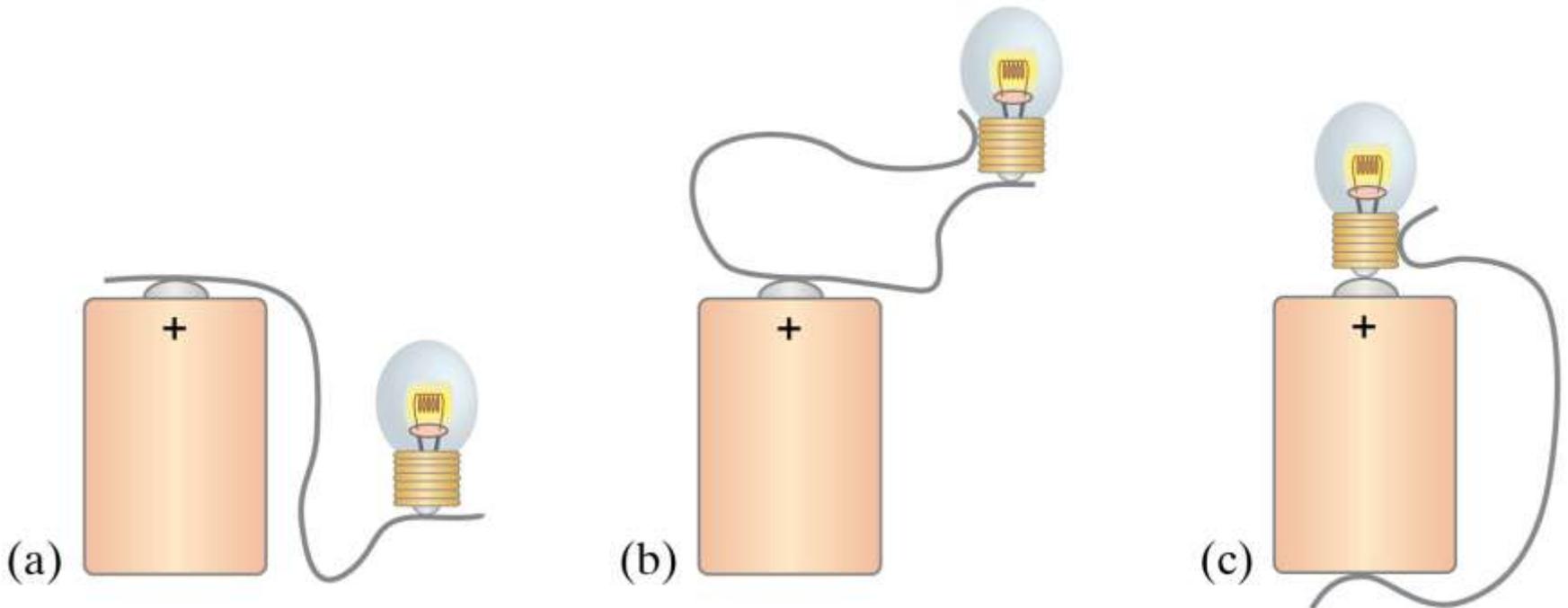
## 18.2 Electric Current

In order for current to flow, there must be a path from one battery terminal, through the circuit, and back to the other battery terminal. Only one of these circuits will work:


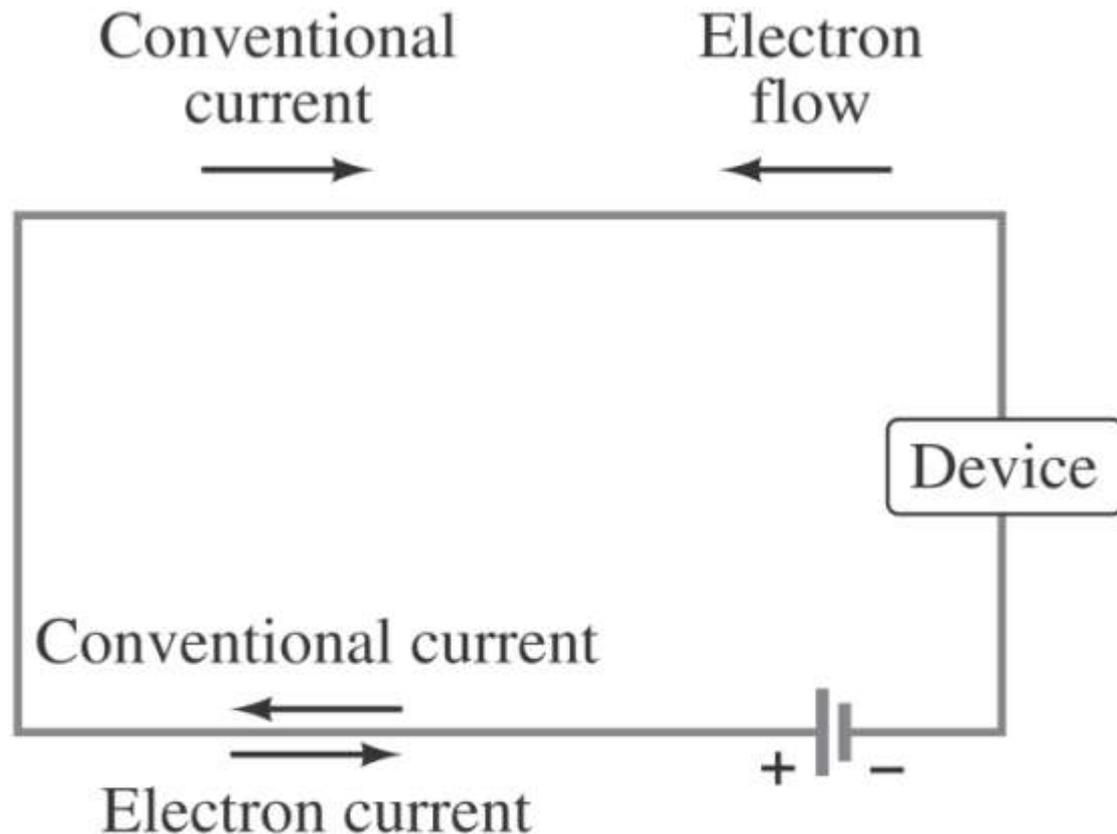
## 18.2 Electric Current

By convention, current is defined as flowing from + to -. Electrons actually flow in the opposite direction, but not all currents consist of electrons.



## 18.3 Ohm's Law: Resistance and Resistors

The ratio of voltage to current is called the resistance:

$$R = \frac{V}{I} \quad (18-2a)$$



$$V = IR \quad (18-2b)$$

# 18.3 Ohm's Law: Resistance and Resistors

In many conductors, the resistance is independent of the voltage; this relationship is called Ohm's law. Materials that do not follow Ohm's law are called nonohmic.

Unit of resistance: the ohm,  $\Omega$ .

$1 \Omega = 1 \text{ V/A}$ .

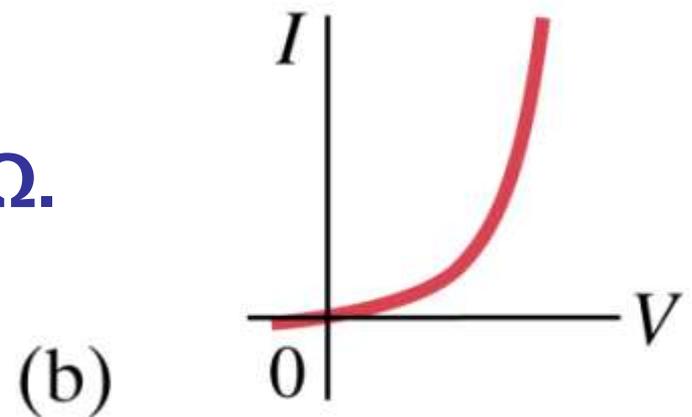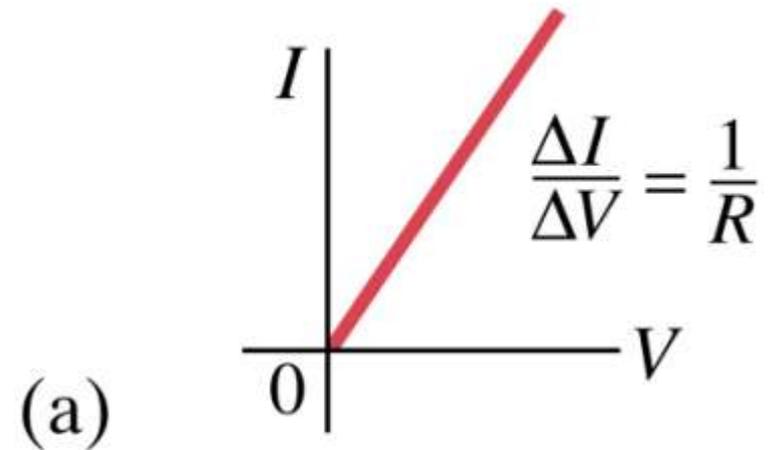


## 18.3 Ohm's Law: Resistance and Resistors



Time for a Gizmo!
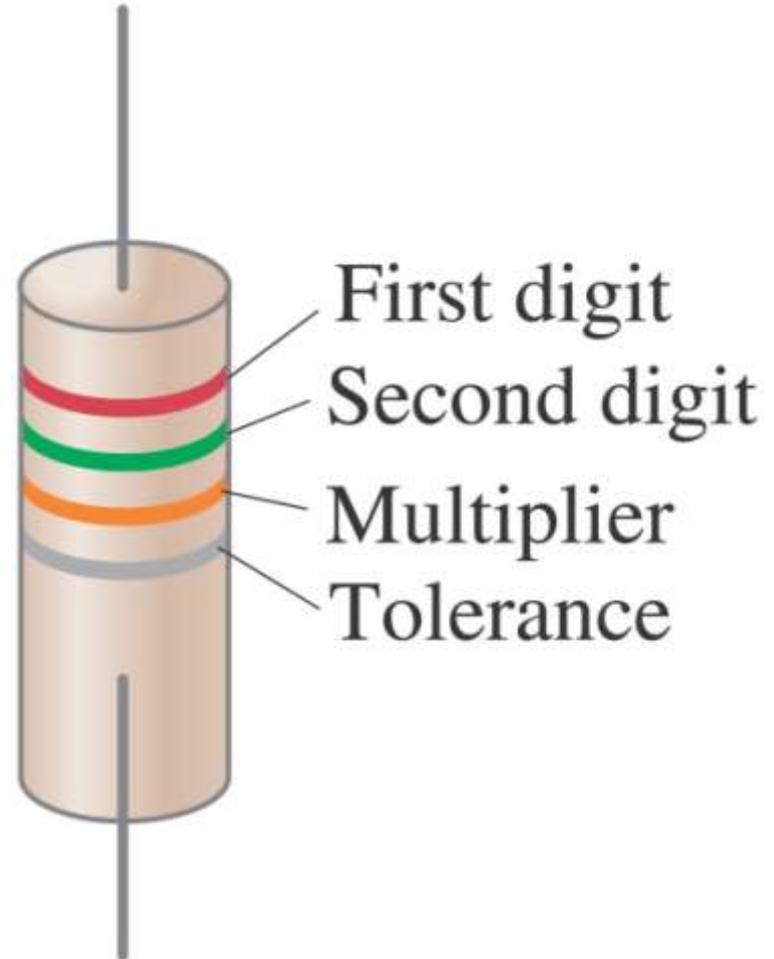
# 18.3 Ohm's Law: Resistance and Resistors

Standard resistors are manufactured for use in electric circuits; they are color-coded to indicate their value and precision.



# **Mnemonic Devices**

**My Very Energetic Mother Just  
Served us Noodles**

**The names of the planets in the solar system, in order from the Sun out: Mercury, Venus, Earth, Mars, Jupiter, Saturn, Uranus, Neptune- Poor Pluto!**

# Mnemonic Devices

## ROY G BIV

The colors of the rainbow in the order of their appearance: **red**, **orange**, **yellow**, **green**, **blue**, **indigo**, and **violet**

# Mnemonic Devices

**Divorced, beheaded, died.**

**Divorced, beheaded, survived**

**For remembering the fates of King Henry VIII's six wives.**

# Mnemonic Devices

## Every Good Boy Deserves Fudge and FACE

In music theory, these represent the notes of the treble (G) clef: the lines (EGBDF) and the spaces (FACE).

# Mnemonic Devices

## HOMES

The names of the Great Lakes:

Huron, Ontario, Michigan, Erie, Superior

# Mnemonic Devices

**ABC**

**CPR Procedure: Airway, Breathing, Circulation**

# **Mnemonic Devices**

**Kings Play Chess On Funny  
Green Squares**

**The Linnean classification system: Kingdom,  
Phylum, Class, Order, Genus, Species**

# 18.3 Ohm's Law: Resistance and Resistors

Resistor Color Code			
Color	Number	Multiplier	Tolerance
Black	0	1	
Brown	1	$10^1$	
Red	2	$10^2$	
Orange	3	$10^3$	
Yellow	4	$10^4$	
Green	5	$10^5$	
Blue	6	$10^6$	
Violet	7	$10^7$	
Gray	8	$10^8$	
White	9	$10^9$	
Gold		$10^{-1}$	5%
Silver		$10^{-2}$	10%
No color			20%

## 18.3 Resistor Code Mnemonic

**B  
B  
R  
O  
Y  
G  
B  
V  
G  
W  
G  
S  
N**

# 18.3 Ohm's Law: Resistance and Resistors

## Some clarifications:

- Batteries maintain a (nearly) constant potential difference; the current varies.
- Resistance is a property of a material or device.
- Current is not a vector but it does have a direction.
- Current and charge do not get used up. Whatever charge goes in one end of a circuit comes out the other end.

## 18.4 Resistivity

The resistance of a wire is directly proportional to its length and inversely proportional to its cross-sectional area:

$$R = \rho \frac{L}{A} \quad (18-3)$$

The constant  $\rho$ , the resistivity, is characteristic of the material.

# 18.4 Resistivity



Time for a Gizmo!

# 18.4 Resistivity

**TABLE 18–1 Resistivity and Temperature Coefficients (at 20°C)**

Material	Resistivity, $\rho$ ( $\Omega \cdot \text{m}$ )	Temperature Coefficient, $\alpha$ ( $^{\circ}\text{C}^{-1}$ )
<i>Conductors</i>		
Silver	$1.59 \times 10^{-8}$	0.0061
Copper	$1.68 \times 10^{-8}$	0.0068
Gold	$2.44 \times 10^{-8}$	0.0034
Aluminum	$2.65 \times 10^{-8}$	0.00429
Tungsten	$5.6 \times 10^{-8}$	0.0045
Iron	$9.71 \times 10^{-8}$	0.00651
Platinum	$10.6 \times 10^{-8}$	0.003927
Mercury	$98 \times 10^{-8}$	0.0009
Nichrome (Ni, Fe, Cr alloy)	$100 \times 10^{-8}$	0.0004
<i>Semiconductors</i> <sup>†</sup>		
Carbon (graphite)	$(3-60) \times 10^{-5}$	-0.0005
Germanium	$(1-500) \times 10^{-3}$	-0.05
Silicon	0 .1-60	-0.07
<i>Insulators</i>		
Glass	$10^9 - 10^{12}$	
Hard rubber	$10^{13} - 10^{15}$	

<sup>†</sup> Values depend strongly on the presence of even slight amounts of impurities.

## 18.4 Resistivity

**For any given material, the resistivity increases with temperature:**

$$\rho_T = \rho_0 [1 + \alpha(T - T_0)] \quad (18-4)$$

**Semiconductors are complex materials, and may have resistivities that decrease with temperature.**

## 18.5 Electric Power

Power, as in kinematics, is the energy transformed by a device per unit time:

$$P = \frac{\text{energy transformed}}{\text{time}} = \frac{QV}{t}$$

$$P = IV$$

(18-5)

# 18.5 Electric Power

The unit of power is the watt, W.

For ohmic devices, we can make the substitutions:

$$P = IV = I(IR) = I^2R \quad (18-6a)$$

$$P = IV = \left(\frac{V}{R}\right)V = \frac{V^2}{R} \quad (18-6b)$$

## 18.5 Electric Power

What you pay for on your electric bill is not power, but energy – the power consumption multiplied by the time.

We have been measuring energy in joules, but the electric company measures it in kilowatt-hours, kWh.

$$\text{One kWh} = (1000 \text{ W})(3600 \text{ s}) = 3.60 \times 10^6 \text{ J}$$


## 18.6 Power in Household Circuits

The wires used in homes to carry electricity have very low resistance. However, if the current is high enough, the power will increase and the wires can become hot enough to start a fire.

To avoid this, we use fuses or circuit breakers, which disconnect when the current goes above a predetermined value.
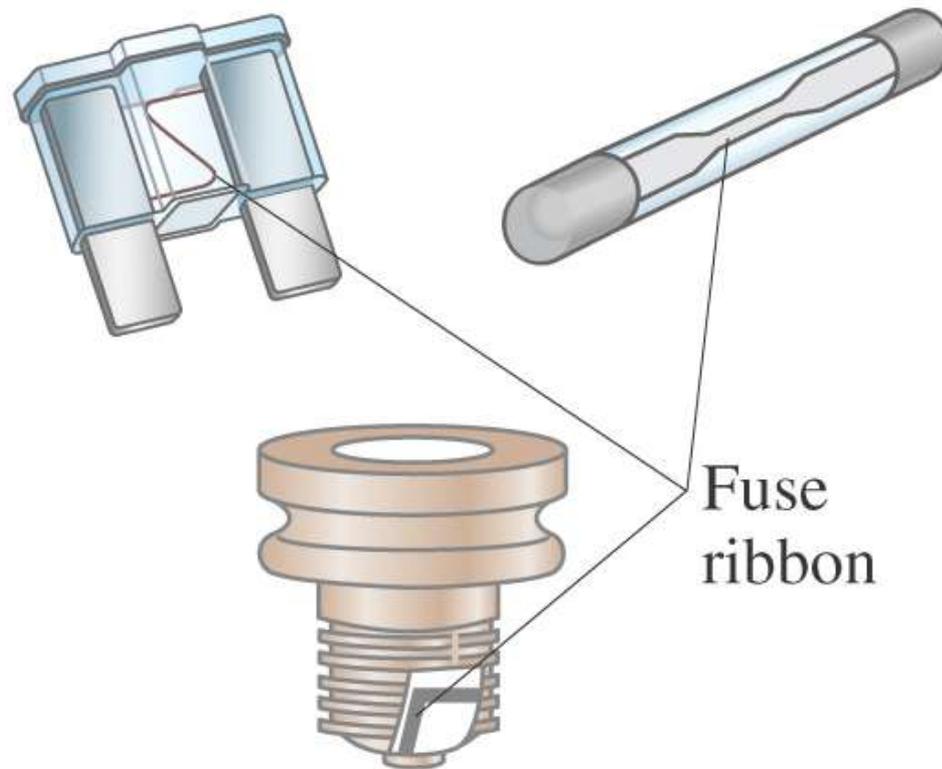
## 18.6 Power in Household Circuits


Fuses are one-use items – if they blow, the fuse is destroyed and must be replaced.




(a) Types of fuses
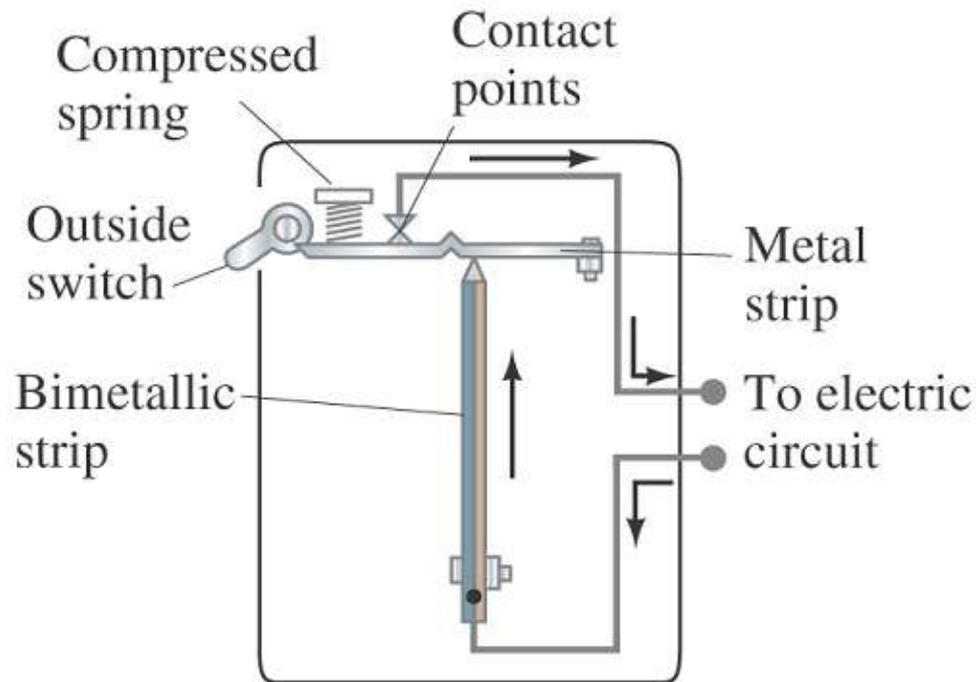
## 18.6 Power in Household Circuits

Circuit breakers, which are now much more common in homes than they once were, are switches that will open if the current is too high; they can then be reset.




(b) Circuit breaker (closed)

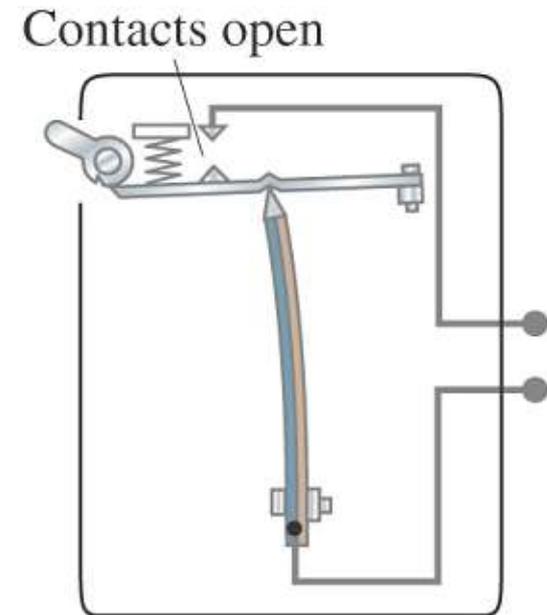


(c) Circuit breaker (open)

# 18.7 Alternating Current

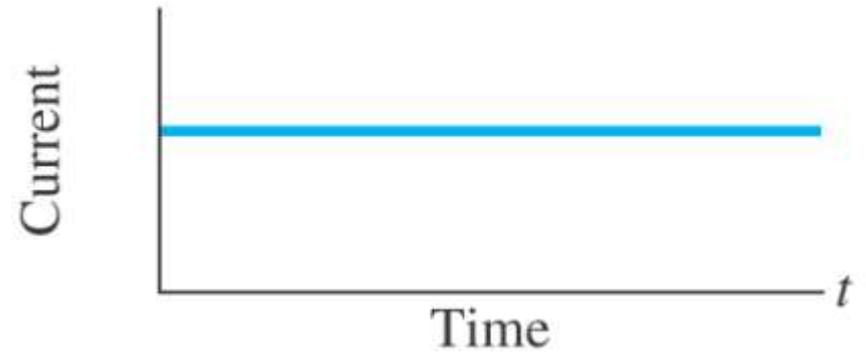**Current from a battery flows steadily in one direction (direct current, DC). Current from a power plant varies sinusoidally (alternating current, AC).**



(a) DC

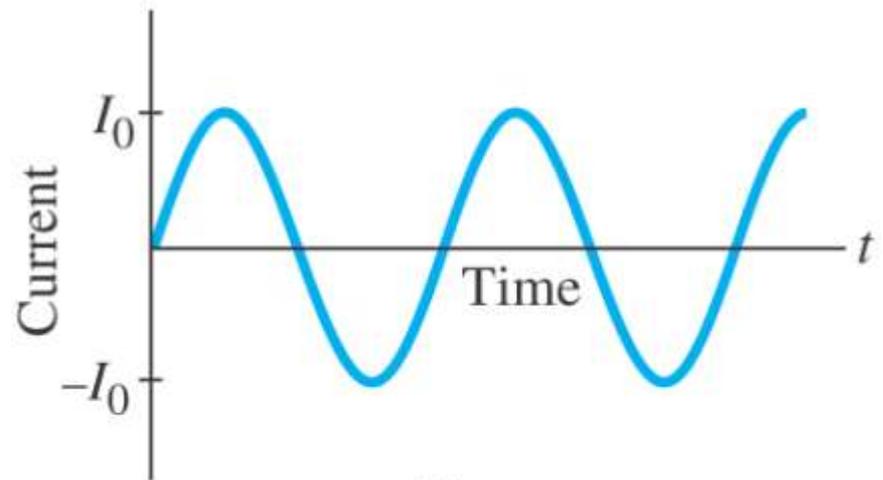

(b) AC

## 18.7 Alternating Current



Time for a Gizmo!

## 18.7 Alternating Current

The voltage varies sinusoidally with time:

$$V = V_0 \sin 2\pi ft = V_0 \sin \omega t$$


as does the current:

$$I = \frac{V}{R} = \frac{V_0}{R} \sin \omega t = I_0 \sin \omega t \quad (18-7)$$

# 18.7 Alternating Current

Multiplying the current and the voltage gives the power:

$$P = I^2 R = I_0^2 R \sin^2 \omega t$$

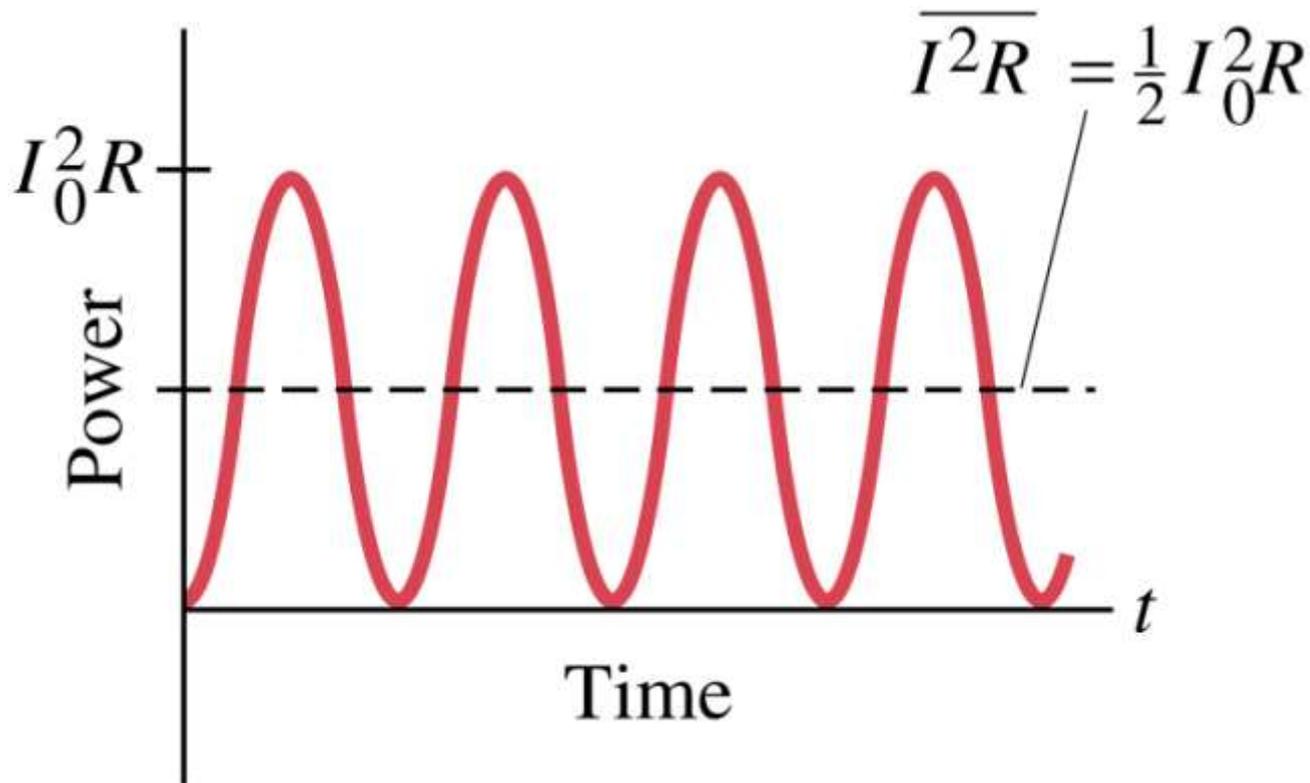

# 18.7 Alternating Current

Usually we are interested in the average power:

$$\bar{P} = \frac{1}{2} I_0^2 R$$

$$\bar{P} = \frac{1}{2} \frac{V_0^2}{R}$$

## 18.7 Alternating Current

The current and voltage both have average values of zero, so we square them, take the average, then take the square root, yielding the root mean square (rms) value.

$$I_{\text{rms}} = \sqrt{\overline{I^2}} = \frac{I_0}{\sqrt{2}} = 0.707I_0 \quad (18-8a)$$

$$V_{\text{rms}} = \sqrt{\overline{V^2}} = \frac{V_0}{\sqrt{2}} = 0.707V_0 \quad (18-8b)$$

# Conductivity Movie