

ConcepTest PowerPoints

Chapter 19

Physics: Principles with Applications, 6th edition

Giancoli

© 2005 Pearson Prentice Hall


This work is protected by United States copyright laws and is provided solely for the use of instructors in teaching their courses and assessing student learning. Dissemination or sale of any part of this work (including on the World Wide Web) will destroy the integrity of the work and is not permitted. The work and materials from it should never be made available to students except by instructors using the accompanying text in their classes. All recipients of this work are expected to abide by these restrictions and to honor the intended pedagogical purposes and the needs of other instructors who rely on these materials.

ConceptTest 19.1a

Series Resistors I

Assume that the voltage of the battery is **9 V** and that the three resistors are **identical**. What is the potential difference across each resistor?

- 1) 12 V
- 2) zero
- 3) 3 V
- 4) 4 V
- 5) you need to know the actual value of R

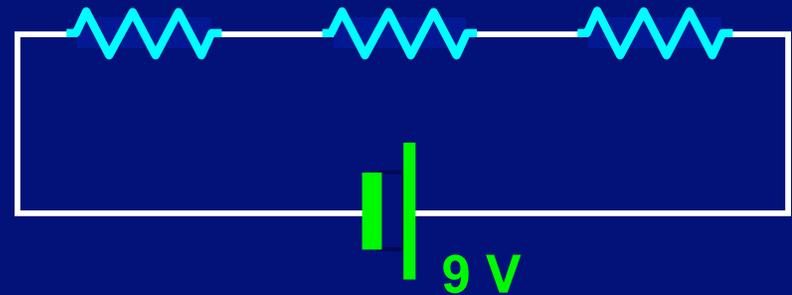

ConceptTest 19.1a

Series Resistors I

Assume that the voltage of the battery is **9 V** and that the three resistors are **identical**. What is the potential difference across each resistor?

1) 12 V


2) zero

3) 3 V

4) 4 V

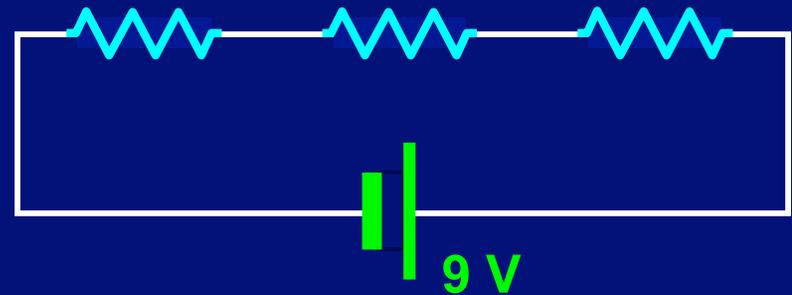5) you need to know the actual value of R

Since the resistors are all equal, the voltage will drop evenly across the 3 resistors, with $1/3$ of 9 V across each one. So we get a 3 V drop across each.




Follow-up: What would be the potential difference if $R = 1 \Omega, 2 \Omega, 3 \Omega$

ConceptTest 19.1b

Series Resistors II

In the circuit below, what is the voltage across R_1 ?

- 1) 12 V
- 2) zero
- 3) 6 V
- 4) 8 V
- 5) 4 V

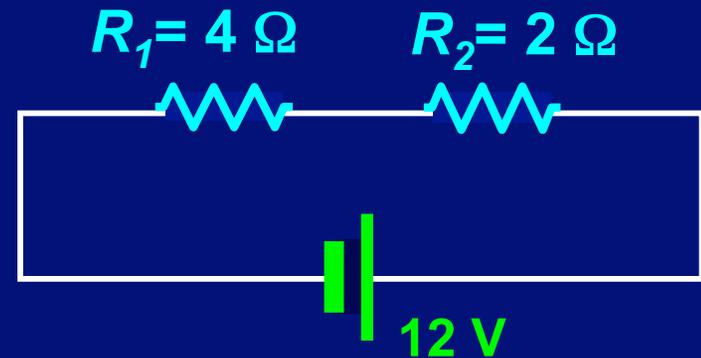

ConceptTest 19.1b

Series Resistors II

In the circuit below, what is the voltage across R_1 ?

1) 12 V


2) zero

3) 6 V

4) 8 V

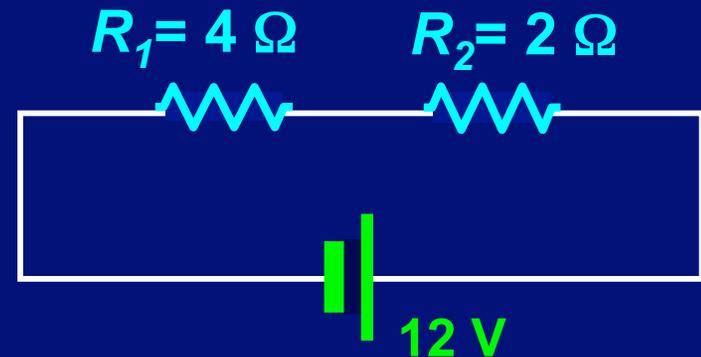5) 4 V

The voltage drop across R_1 has to be twice as big as the drop across R_2 . This means that $V_1 = 8 \text{ V}$ and $V_2 = 4 \text{ V}$. Or else you could find the current $I = V/R = (12 \text{ V})/(6 \Omega) = 2 \text{ A}$, then use Ohm's Law to get voltages.




Follow-up: What happens if the voltage is doubled?

ConceptTest 19.2a

Parallel Resistors I

In the circuit below, what is the current through R_1 ?

- 1) 10 A
- 2) zero
- 3) 5 A
- 4) 2 A
- 5) 7 A

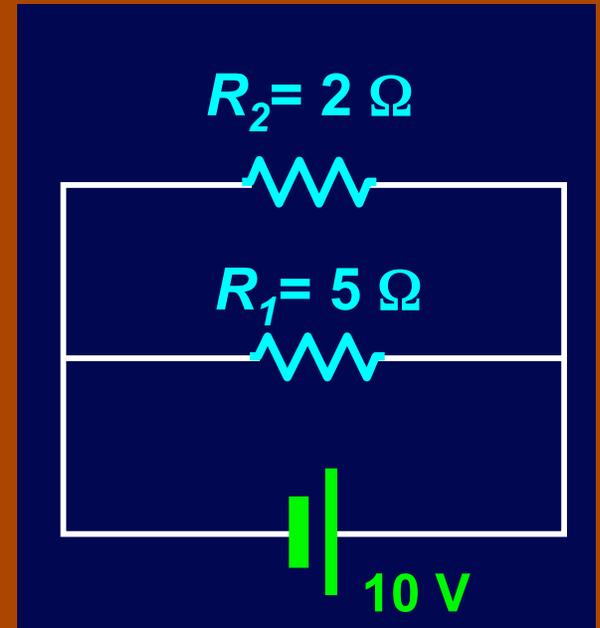

ConceptTest 19.2a

Parallel Resistors I

In the circuit below, what is the current through R_1 ?

1) 10 A


2) zero

3) 5 A

4) 2 A

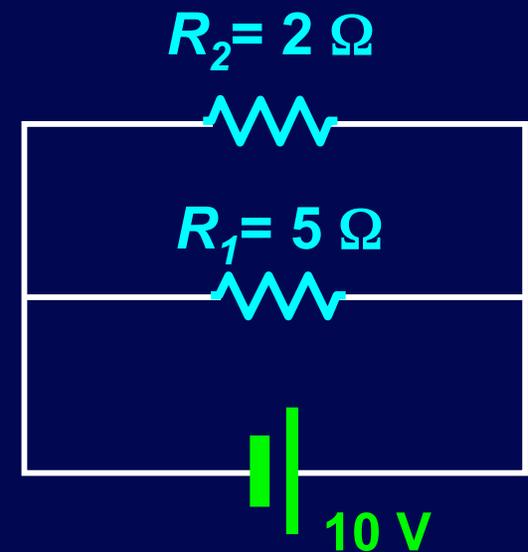5) 7 A

The **voltage** is the **same** (10 V) across each resistor because they are in parallel. Thus, we can use Ohm's Law, $V_1 = I_1 R_1$ to find the current $I_1 = 2$ A.




Follow-up: What is the total current through the battery?

ConceptTest 19.2b

Parallel Resistors II

Points P and Q are connected to a battery of fixed voltage. As more resistors R are added to the parallel circuit, what happens to the **total current** in the circuit?

- 1) increases
- 2) remains the same
- 3) decreases
- 4) drops to zero

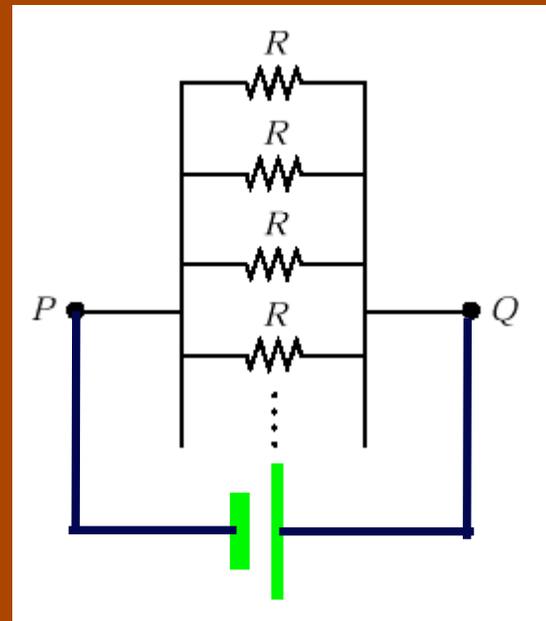


ConceptTest 19.2b

Parallel Resistors II

Points P and Q are connected to a battery of fixed voltage. As more resistors R are added to the parallel circuit, what happens to the **total current** in the circuit?

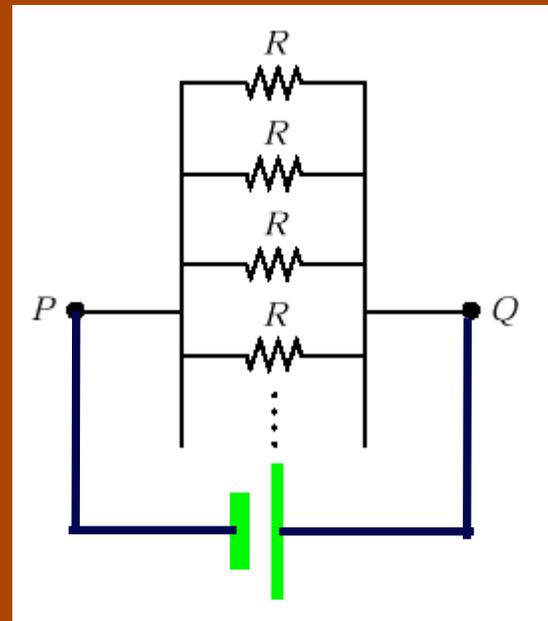- 1) **increases**
- 2) **remains the same**
- 3) **decreases**
- 4) **drops to zero**

As we add parallel resistors, the overall resistance of the circuit drops. Since $V = IR$, and V is held constant by the battery, when resistance decreases, the current must increase.




Follow-up: What happens to the current through each resistor?

ConceptTest 19.3a

Short Circuit

Current flows through a lightbulb. If a wire is now connected across the bulb, what happens?

- 1) all the current continues to flow through the bulb
- 2) half the current flows through the wire, the other half continues through the bulb
- 3) all the current flows through the wire
- 4) none of the above

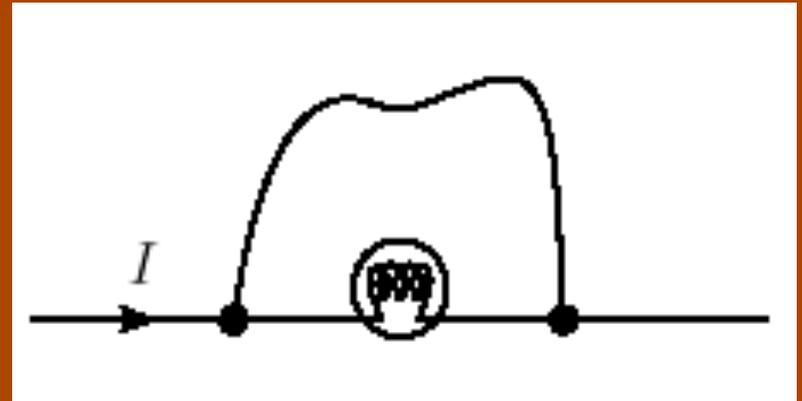


ConceptTest 19.3a

Short Circuit

Current flows through a lightbulb. If a wire is now connected across the bulb, what happens?

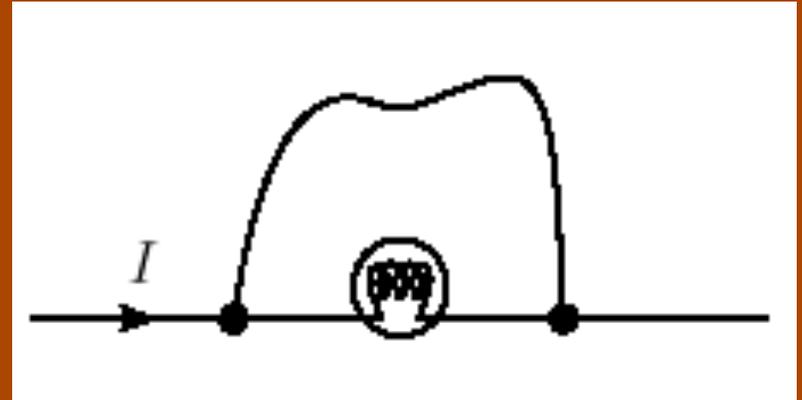- 1) all the current continues to flow through the bulb
- 2) half the current flows through the wire, the other half continues through the bulb
- 3) all the current flows through the wire
- 4) none of the above

The current divides based on the ratio of the resistances. If one of the resistances is zero, then **ALL** of the current will flow through that path.




Follow-up: Doesn't the wire have SOME resistance?

ConceptTest 19.3b

Short Circuit II

Two lightbulbs A and B are connected in series to a constant voltage source. When a wire is connected across B, bulb A will:

- 1) glow brighter than before
- 2) glow just the same as before
- 3) glow dimmer than before
- 4) go out completely
- 5) explode

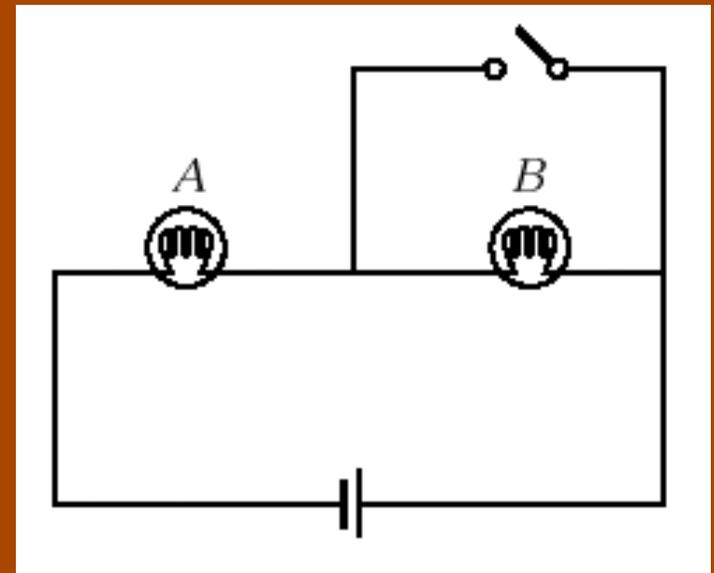


ConceptTest 19.3b

Short Circuit II

Two lightbulbs A and B are connected in series to a constant voltage source. When a wire is connected across B, bulb A will:

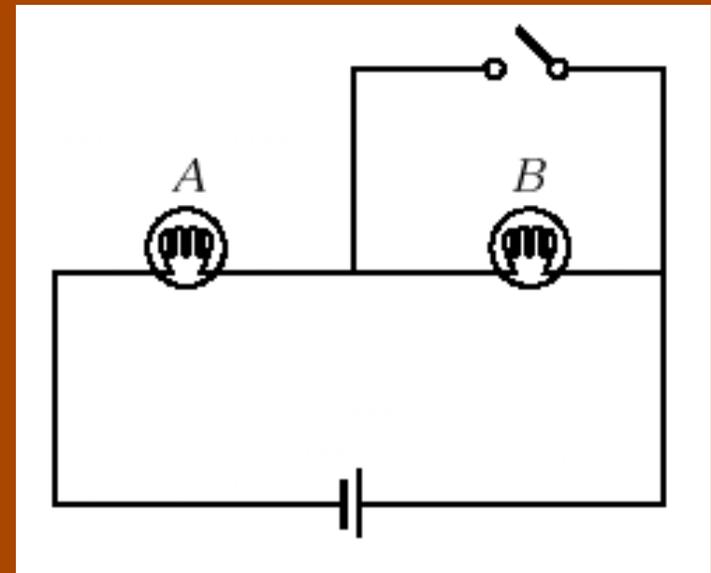- 1) glow brighter than before
- 2) glow just the same as before
- 3) glow dimmer than before
- 4) go out completely
- 5) explode

Since bulb B is bypassed by the wire, the total resistance of the circuit decreases. This means that the current through bulb A increases.




Follow-up: What happens to bulb B?

ConceptTest 19.4a

Circuits I

The lightbulbs in the circuit below are identical with the same resistance R . Which circuit produces more light? (brightness \iff power)

- 1) circuit 1
- 2) circuit 2
- 3) both the same
- 4) it depends on R

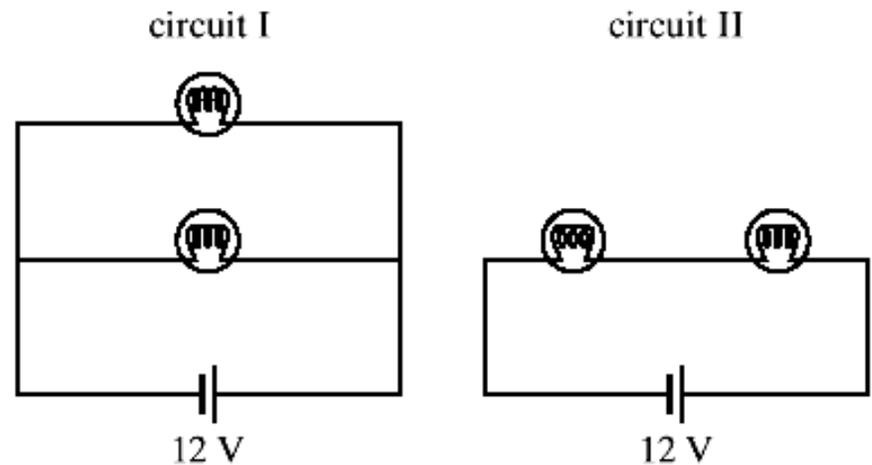


ConceptTest 19.4a

Circuits I

The lightbulbs in the circuit below are identical with the same resistance R . Which circuit produces more light? (brightness \iff power)

- 1) circuit 1
- 2) circuit 2
- 3) both the same
- 4) it depends on R

In #1, the bulbs are in parallel, lowering the total resistance of the circuit. Thus, circuit #1 will draw a higher current, which leads to more light, because $P = IV$.

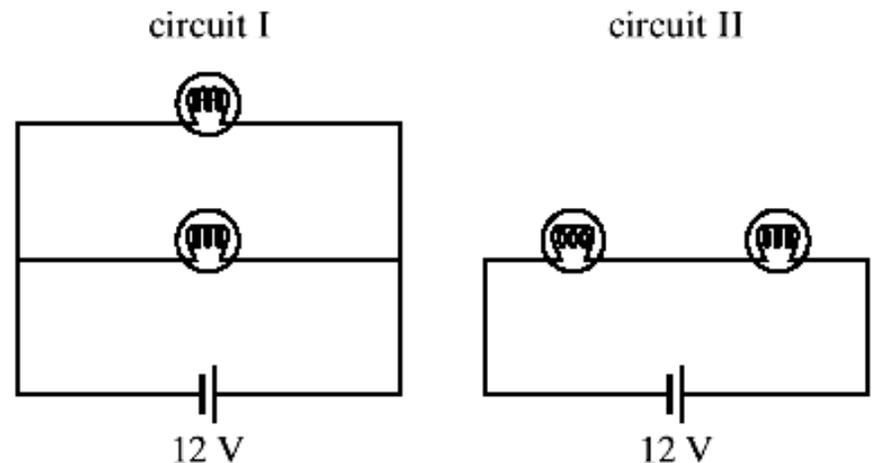


ConceptTest 19.4b

Circuits II

The three lightbulbs in the circuit all have the **same resistance of $1\ \Omega$** . By how much is the **brightness of bulb B** greater or smaller than the **brightness of bulb A**? (brightness \iff power)

- 1) **twice as much**
- 2) **the same**
- 3) **$1/2$ as much**
- 4) **$1/4$ as much**
- 5) **4 times as much**

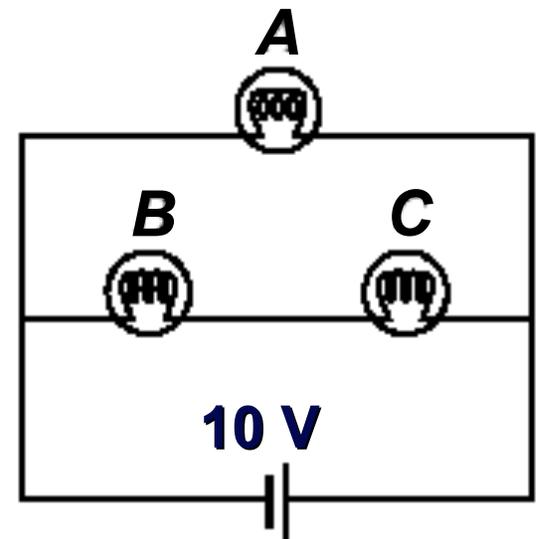

ConceptTest 19.4b

Circuits II


The three light bulbs in the circuit all have the **same resistance of $1\ \Omega$** . By how much is the **brightness of bulb B** greater or smaller than the **brightness of bulb A**? (brightness \iff power)

- 1) twice as much
- 2) the same
- 3) $1/2$ as much
- 4) $1/4$ as much
- 5) 4 times as much

We can use $P = V^2/R$ to compare the power:

$$P_A = (V_A)^2/R_A = (10\ \text{V})^2/1\ \Omega = 100\ \text{W}$$
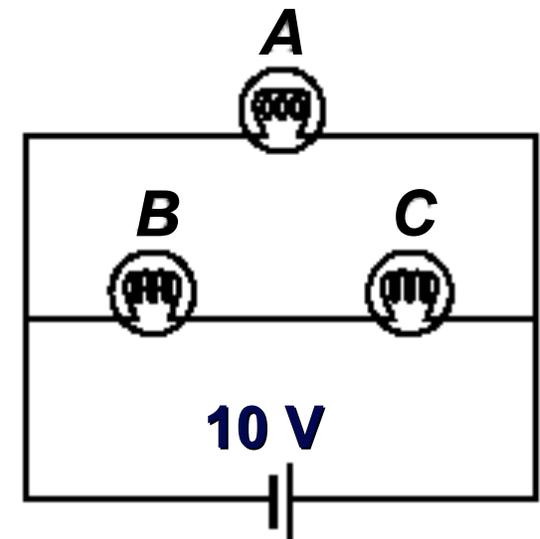
$$P_B = (V_B)^2/R_B = (5\ \text{V})^2/1\ \Omega = 25\ \text{W}$$




Follow-up: What is the total current in the circuit?

ConceptTest 19.5a

More Circuits I

What happens to the voltage across the resistor R_1 when the switch is closed? The voltage will:

- 1) increase
- 2) decrease
- 3) stay the same

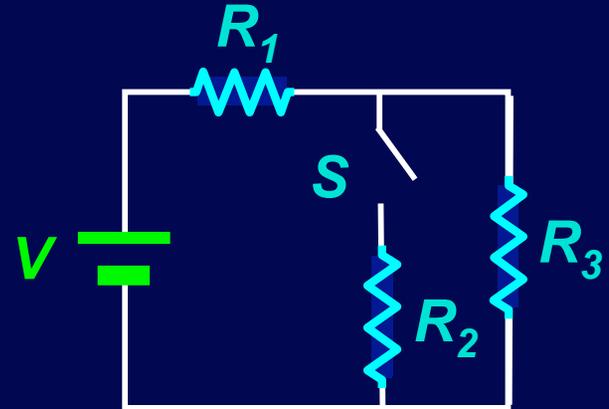


ConceptTest 19.5a

More Circuits I

What happens to the voltage across the resistor R_1 when the switch is closed? The voltage will:

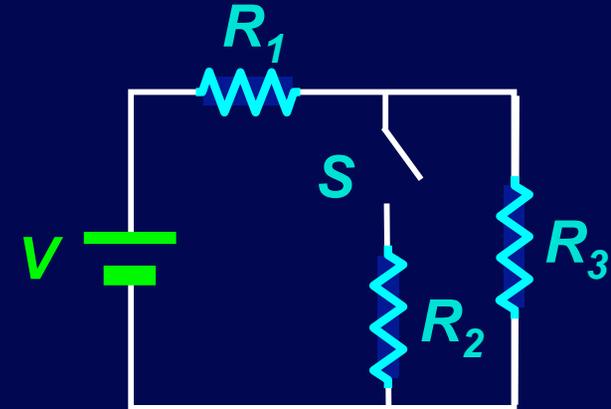- 1) increase
- 2) decrease
- 3) stay the same

With the switch closed, the addition of R_2 to R_3 decreases the equivalent resistance, so the current from the battery increases. This will cause an increase in the voltage across R_1 .




Follow-up: What happens to the current through R_3 ?

ConceptTest 19.5b

More Circuits II

What happens to the voltage across the resistor R_4 when the switch is closed?

- 1) increases
- 2) decreases
- 3) stays the same

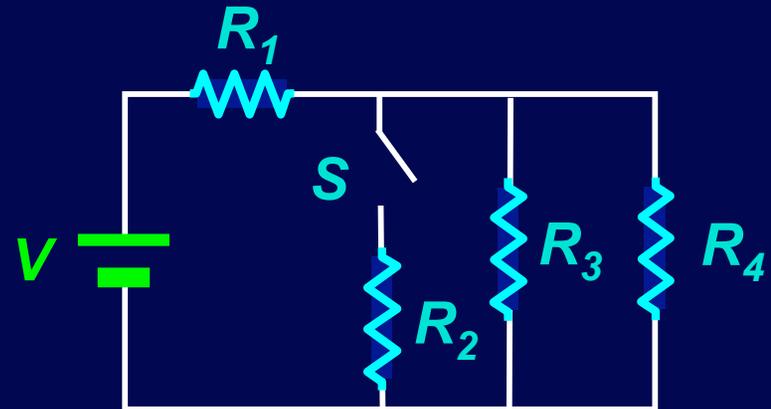

ConceptTest 19.5b

More Circuits II


What happens to the voltage across the resistor R_4 when the switch is closed?

1) increases

2) decreases

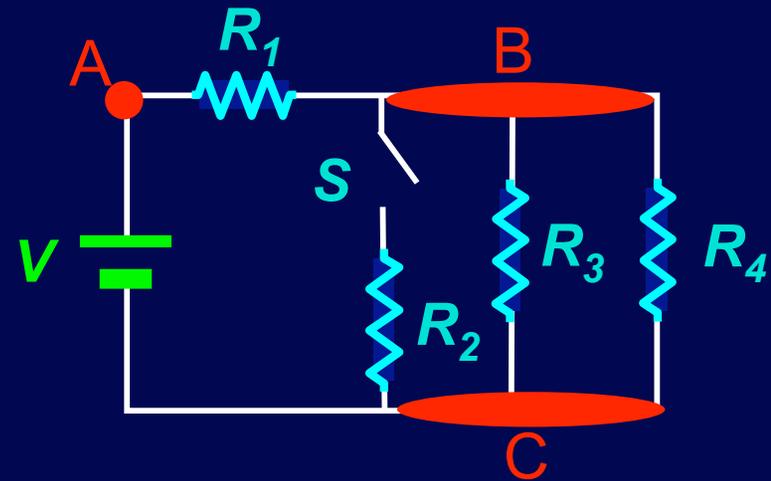3) stays the same

We just saw that closing the switch causes an increase in the voltage across R_1 (which is V_{AB}). The voltage of the battery is constant, so if V_{AB} increases, then V_{BC} must decrease!




Follow-up: What happens to the current through R_4 ?

ConceptTest 19.6

Which resistor has the greatest current going through it? Assume that all the resistors are equal.

Even More Circuits

- 1) R_1
- 2) both R_1 and R_2 equally
- 3) R_3 and R_4
- 4) R_5
- 5) all the same

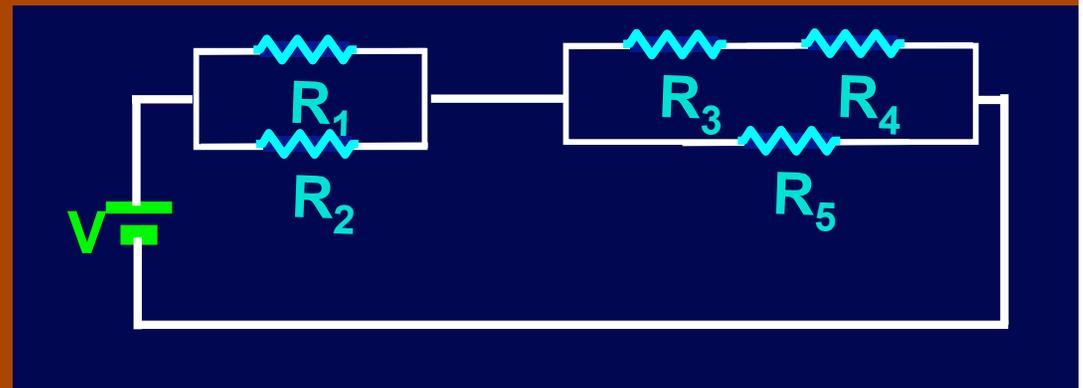


ConceptTest 19.6

Which resistor has the greatest current going through it? Assume that all the resistors are equal.

Even More Circuits

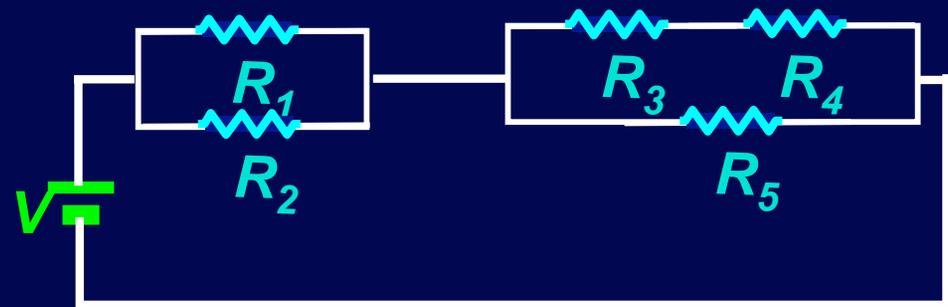- 1) R_1
- 2) both R_1 and R_2 equally
- 3) R_3 and R_4
- 4) R_5
- 5) all the same

The same current must flow through left and right combinations of resistors. On the LEFT, the current splits equally, so $I_1 = I_2$. On the RIGHT, more current will go through R_5 than $R_3 + R_4$ since the branch containing R_5 has less resistance.




Follow-up: Which one has the smallest voltage drop?

ConceptTest 19.7

Junction Rule

What is the current in branch P?

- 1) 2 A
- 2) 3 A
- 3) 5 A
- 4) 6 A
- 5) 10 A

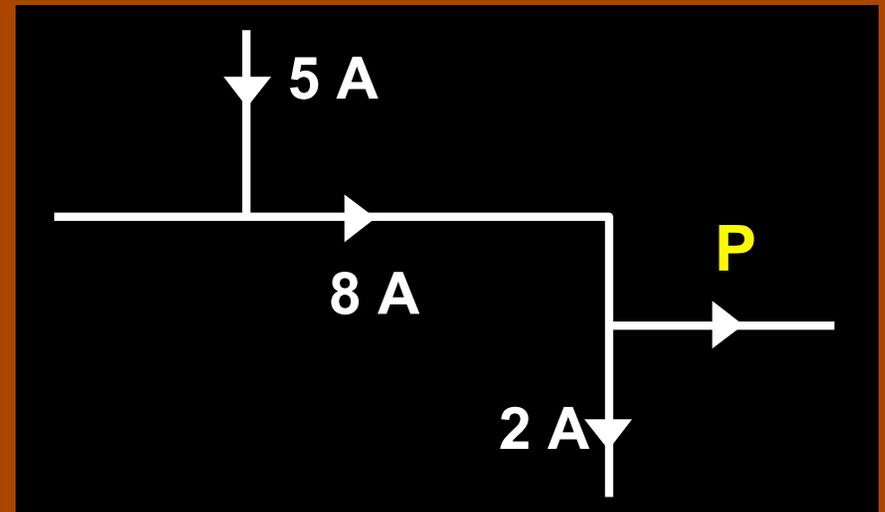

ConceptTest 19.7

What is the current in branch P?

Junction Rule

1) 2 A


2) 3 A

3) 5 A

4) 6 A

5) 10 A

The current entering the junction in red is 8 A, so the current leaving must also be 8 A. One exiting branch has 2 A, so the other branch (at P) must have 6 A.

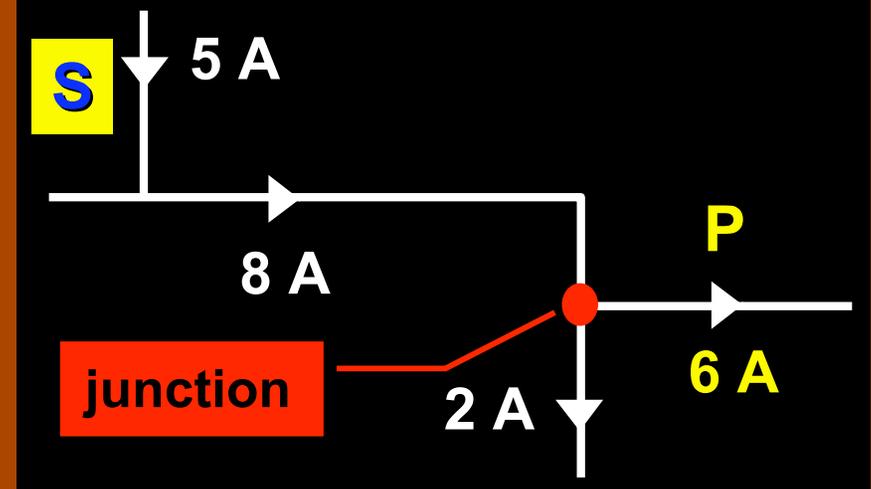


ConceptTest 19.8

Kirchhoff's Rules

The lightbulbs in the circuit are **identical**. When the switch is closed, what happens?

- 1) both bulbs go out
- 2) intensity of both bulbs increases
- 3) intensity of both bulbs decreases
- 4) A gets brighter and B gets dimmer
- 5) nothing changes

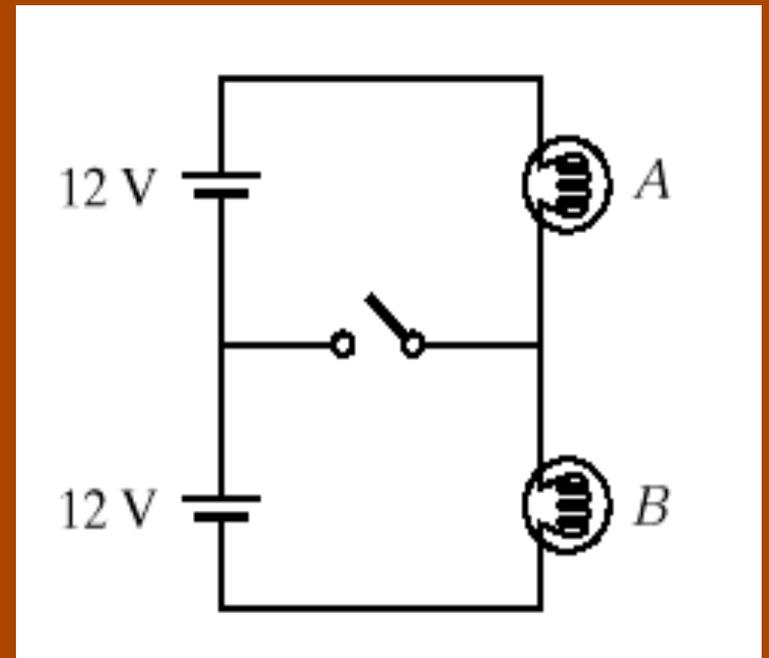

ConceptTest 19.8


Kirchhoff's Rules

The lightbulbs in the circuit are **identical**. When the switch is closed, what happens?

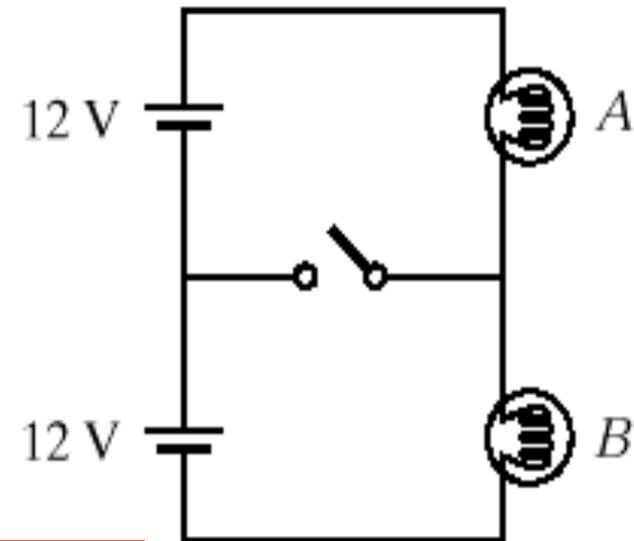- 1) both bulbs go out
- 2) intensity of both bulbs increases
- 3) intensity of both bulbs decreases
- 4) A gets brighter and B gets dimmer
- 5) nothing changes

When the switch is open, the point between the bulbs is at 12 V. But so is the point between the batteries. If there is no potential difference, then no current will flow once the switch is closed!! Thus, nothing changes.

Follow-up: What happens if the bottom battery is replaced by a 24 V battery?




24 V

ConceptTest 19.9

An ammeter A is connected between points *a* and *b* in the circuit below, in which the four resistors are identical. The current through the ammeter is:

Wheatstone Bridge

- 1) I
- 2) $I/2$
- 3) $I/3$
- 4) $I/4$
- 5) zero

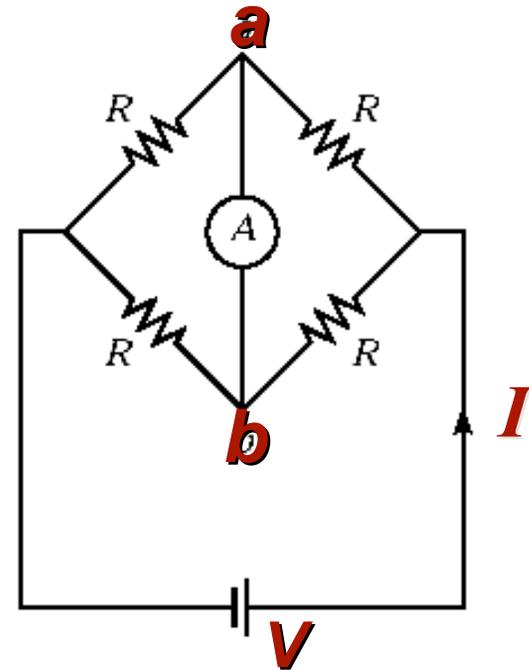


ConceptTest 19.9

An ammeter A is connected between points *a* and *b* in the circuit below, in which the four resistors are identical. The current through the ammeter is:

Wheatstone Bridge

- 1) I
- 2) $I/2$
- 3) $I/3$
- 4) $I/4$
- 5) zero

Since all resistors are identical, the voltage drops are the same across the upper branch and the lower branch. Thus, the potentials at points *a* and *b* are also the same. Therefore, no current flows.

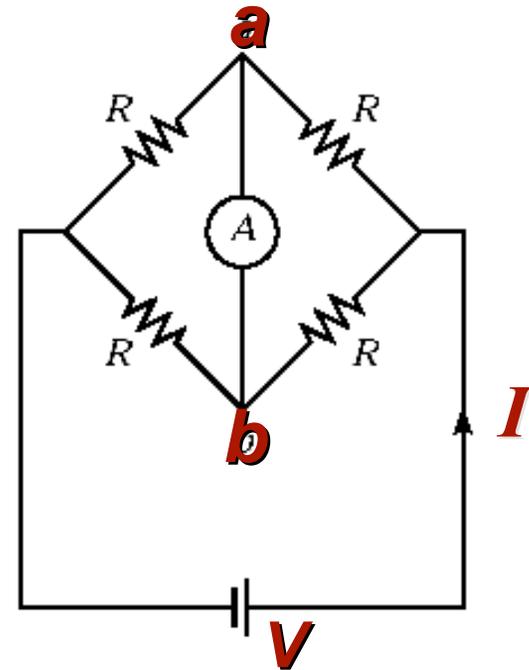


ConceptTest 19.10

Which of the equations is valid for the circuit below?

More Kirchhoff's Rules

- 1) $2 - I_1 - 2I_2 = 0$
- 2) $2 - 2I_1 - 2I_2 - 4I_3 = 0$
- 3) $2 - I_1 - 4 - 2I_2 = 0$
- 4) $I_3 - 4 - 2I_2 + 6 = 0$
- 5) $2 - I_1 - 3I_3 - 6 = 0$

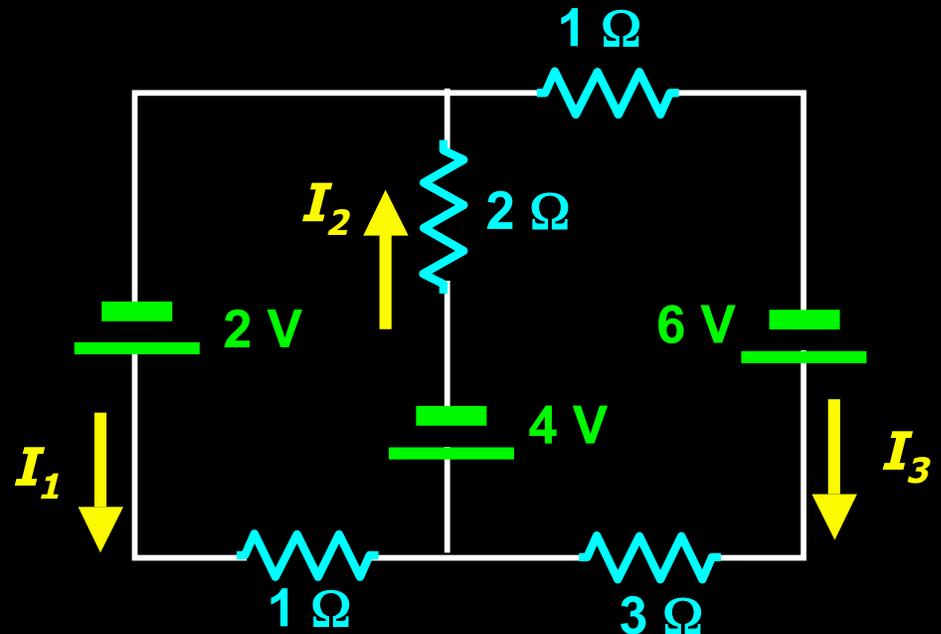

ConceptTest 19.10

Which of the equations is valid for the circuit below?

More Kirchhoff's Rules

1) $2 - I_1 - 2I_2 = 0$


2) $2 - 2I_1 - 2I_2 - 4I_3 = 0$

3) $2 - I_1 - 4 - 2I_2 = 0$

4) $I_3 - 4 - 2I_2 + 6 = 0$

5) $2 - I_1 - 3I_3 - 6 = 0$

Eqn. 3 is valid for the left loop:
The left battery gives +2V, then there is a drop through a 1Ω resistor with current I_1 flowing. Then we go through the middle battery (but from + to -!), which gives -4V. Finally, there is a drop through a 2Ω resistor with current I_2 .

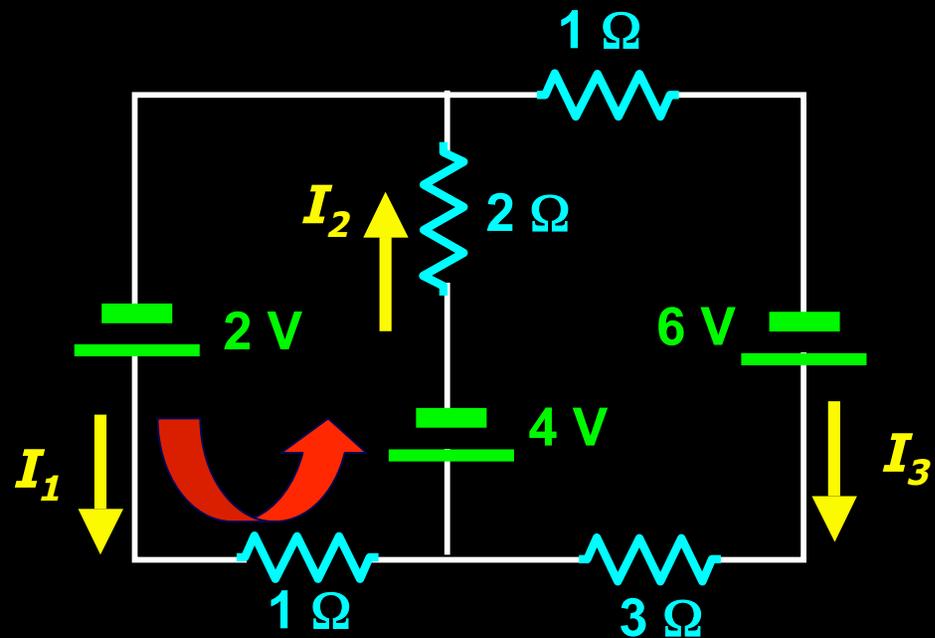

ConceptTest 19.11a

Capacitors I

What is the equivalent capacitance, C_{eq} , of the combination below?

1) $C_{eq} = 3/2 C$


2) $C_{eq} = 2/3 C$

3) $C_{eq} = 3 C$

4) $C_{eq} = 1/3 C$

5) $C_{eq} = 1/2 C$

The 2 equal capacitors in series add up as inverses, giving $1/2 C$. These are parallel to the first one, which add up directly. Thus, the total equivalent capacitance is $3/2 C$.

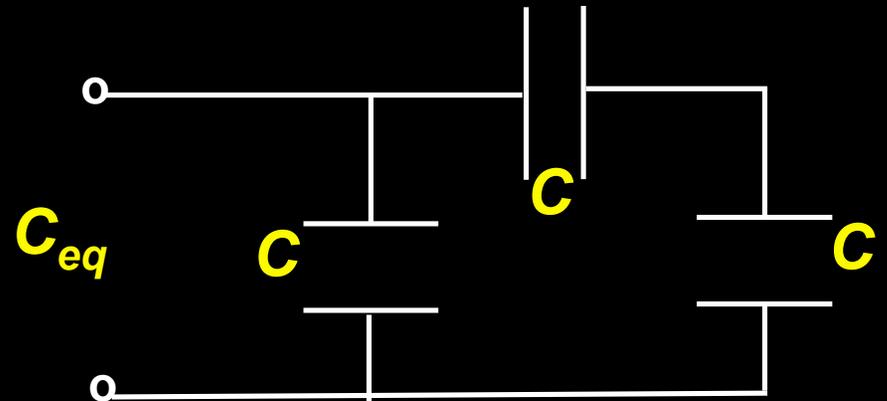


ConceptTest 19.11b

Capacitors II

How does the voltage V_1 across the first capacitor (C_1) compare to the voltage V_2 across the second capacitor (C_2)?

- 1) $V_1 = V_2$
- 2) $V_1 > V_2$
- 3) $V_1 < V_2$
- 4) all voltages are zero

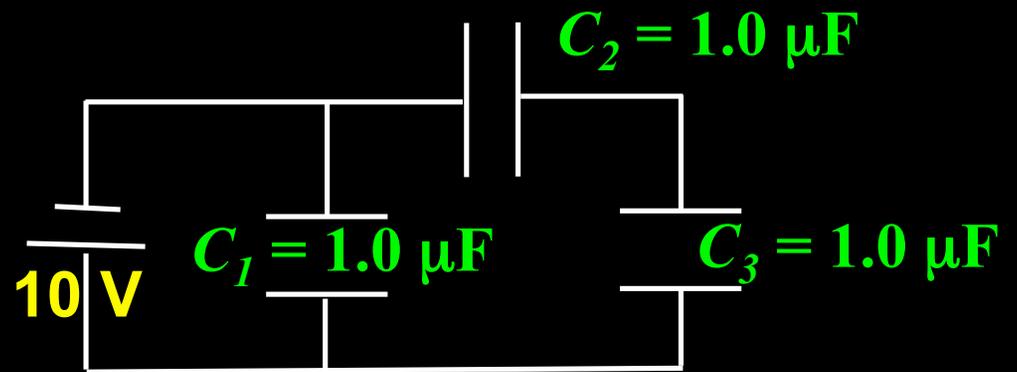

ConceptTest 19.11b

Capacitors II

How does the voltage V_1 across the first capacitor (C_1) compare to the voltage V_2 across the second capacitor (C_2)?


1) $V_1 = V_2$

2) $V_1 > V_2$

3) $V_1 < V_2$

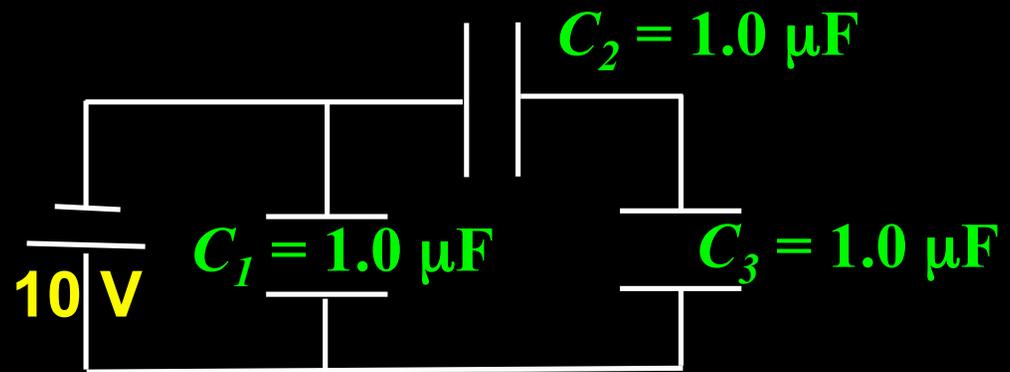4) all voltages are zero

The voltage across C_1 is 10 V. The combined capacitors C_2+C_3 are parallel to C_1 . The voltage across C_2+C_3 is also 10 V. Since C_2 and C_3 are in series, their voltages add. Thus the voltage across C_2 and C_3 each has to be 5 V, which is less than V_1 .




Follow-up: What is the current in this circuit?

ConceptTest 19.11c

Capacitors III

How does the charge Q_1 on the first capacitor (C_1) compare to the charge Q_2 on the second capacitor (C_2)?

- 1) $Q_1 = Q_2$
- 2) $Q_1 > Q_2$
- 3) $Q_1 < Q_2$
- 4) all charges are zero

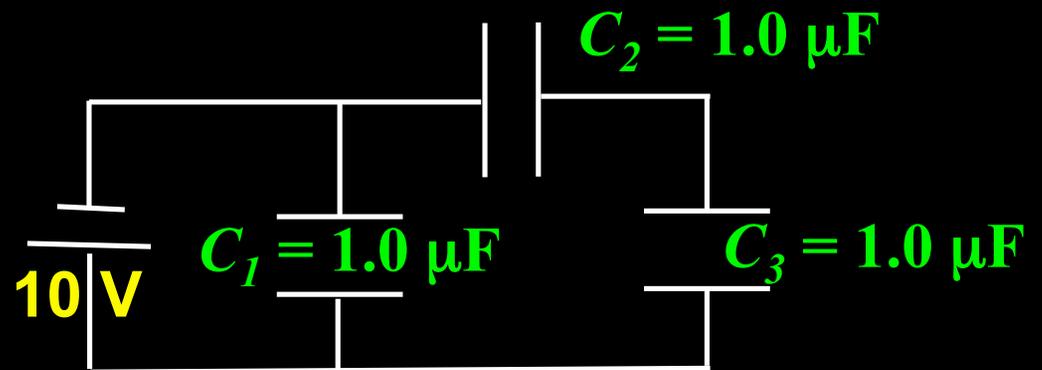

ConceptTest 19.11c

Capacitors III

How does the charge Q_1 on the first capacitor (C_1) compare to the charge Q_2 on the second capacitor (C_2)?

1) $Q_1 = Q_2$

2) $Q_1 > Q_2$

3) $Q_1 < Q_2$

4) all charges are zero

We already know that the voltage across C_1 is 10 V and the voltage across C_2 and C_3 each is 5 V. Since $Q = CV$ and C is the same for all the capacitors, then since $V_1 > V_2$ therefore $Q_1 > Q_2$.

