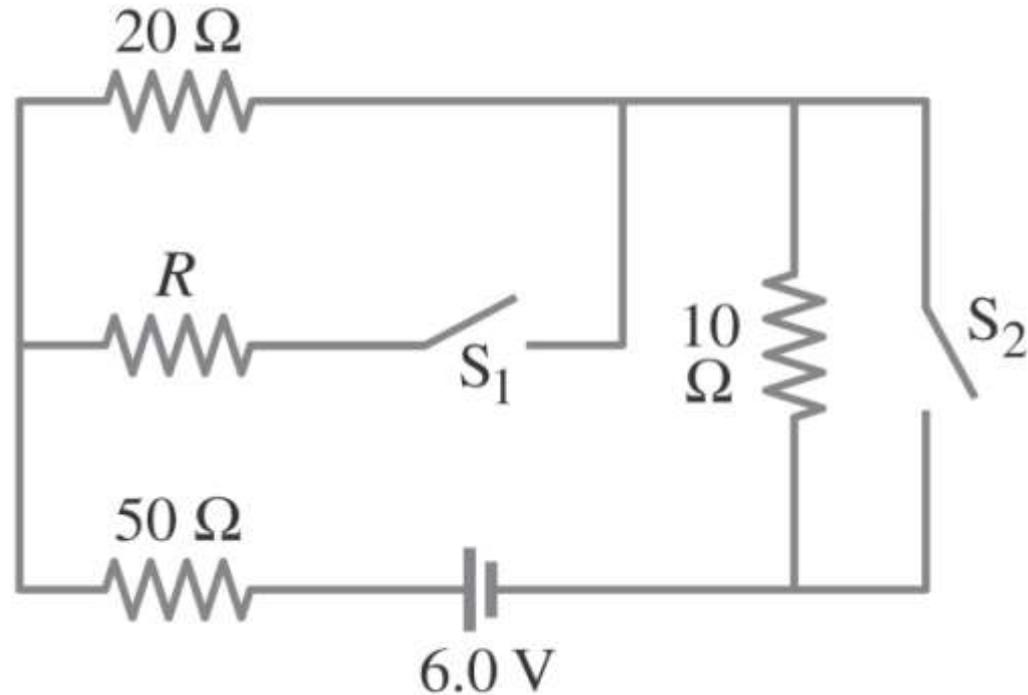


# Chapter 19

## DC Circuits



# 19.1 EMF and Terminal Voltage


Electric circuit needs battery or generator to produce current – these are called sources of emf.

Battery is a nearly constant voltage source, but does have a small internal resistance, which reduces the actual voltage from the ideal emf:

$$V_{ab} = \mathcal{E} - Ir \quad (19-1)$$

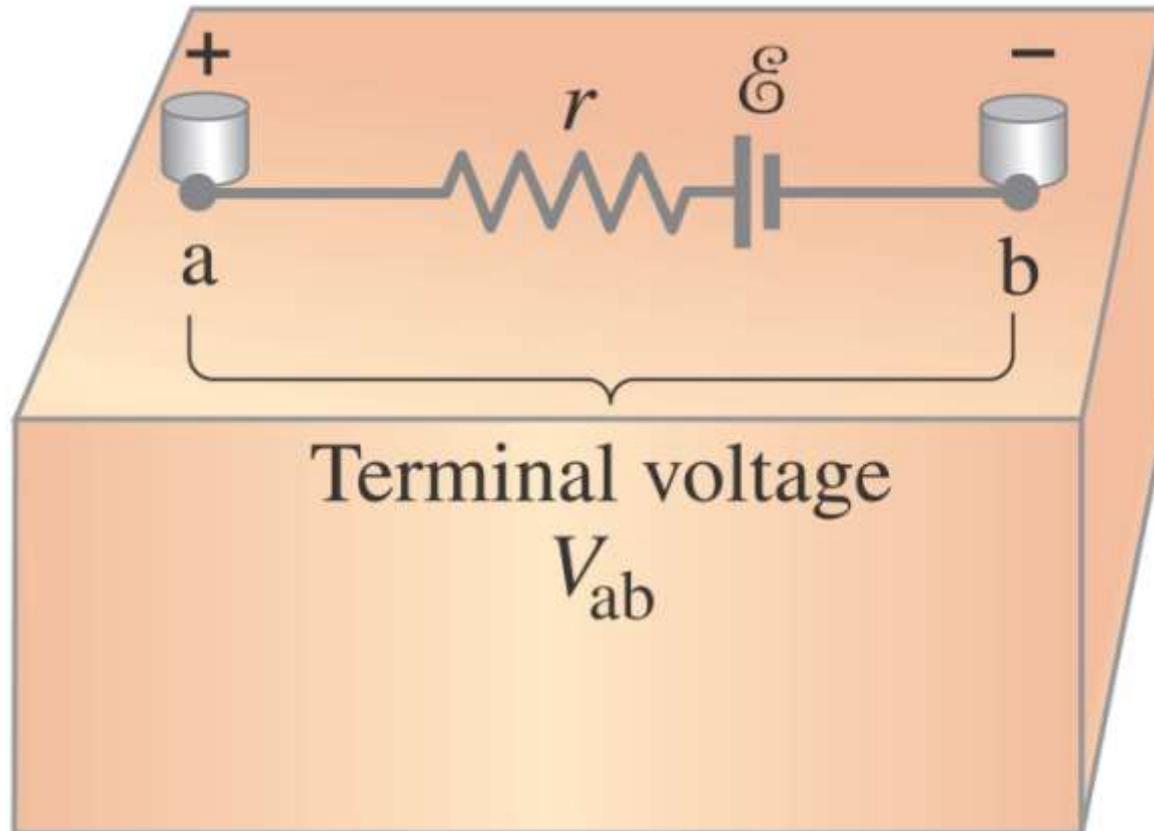
## 19.1 EMF and Terminal Voltage

This resistance behaves as though it were in series with the emf.


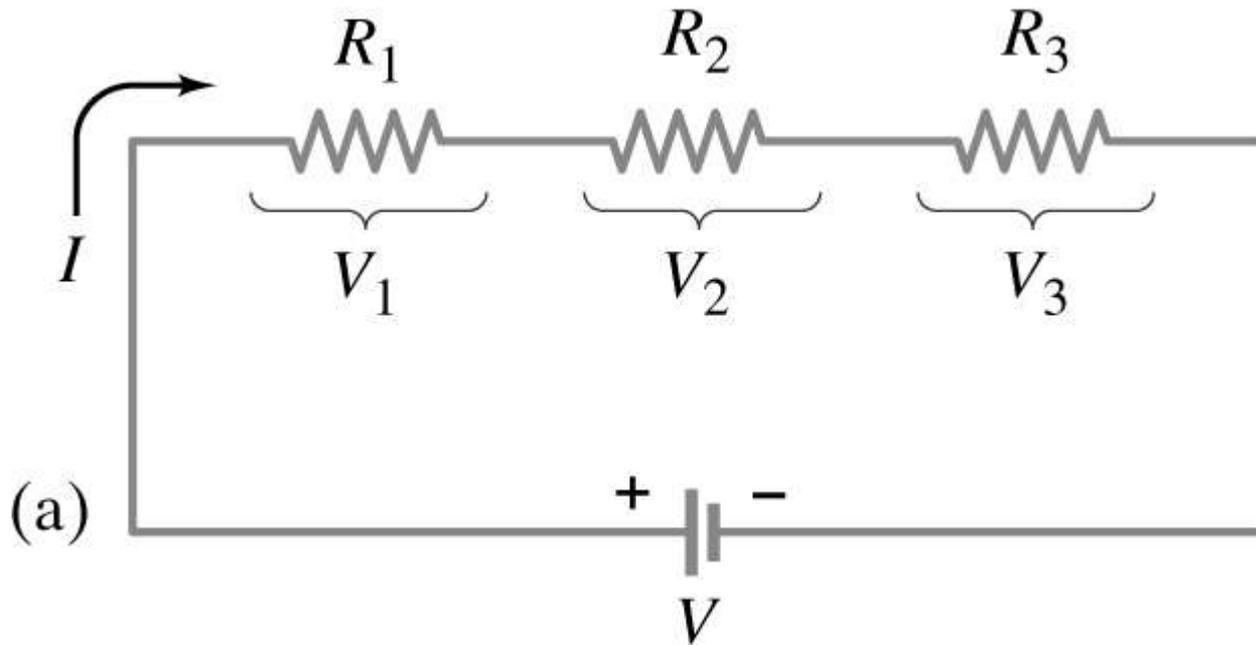
## 19.2 Resistors in Series and in Parallel

A series connection has a single path from the battery, through each circuit element in turn, then back to the battery.



## 19.2 Resistors in Series and in Parallel


The current through each resistor is the same; the voltage depends on the resistance. The sum of the voltage drops across the resistors equals the battery voltage.

$$V = V_1 + V_2 + V_3 = IR_1 + IR_2 + IR_3 \quad (19-2)$$
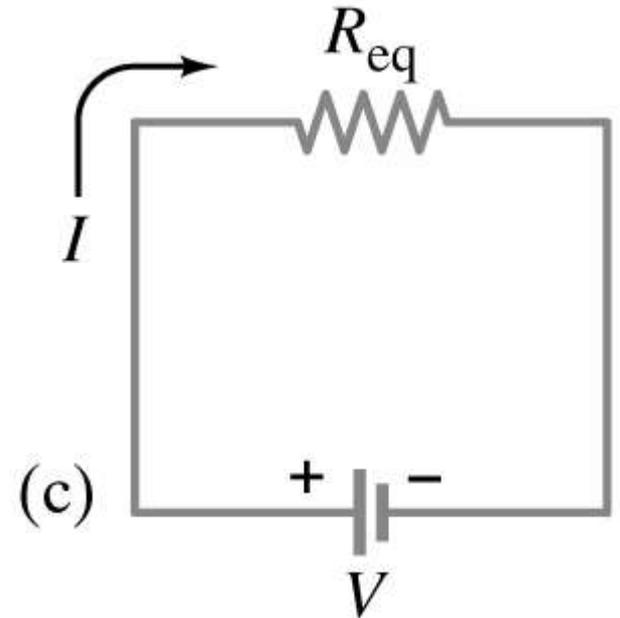
## 19.2 Resistors in Series and in Parallel


From this we get the equivalent resistance (that single resistance that gives the same current in the circuit).

$$R_{\text{eq}} = R_1 + R_2 + R_3 \quad (19-3)$$


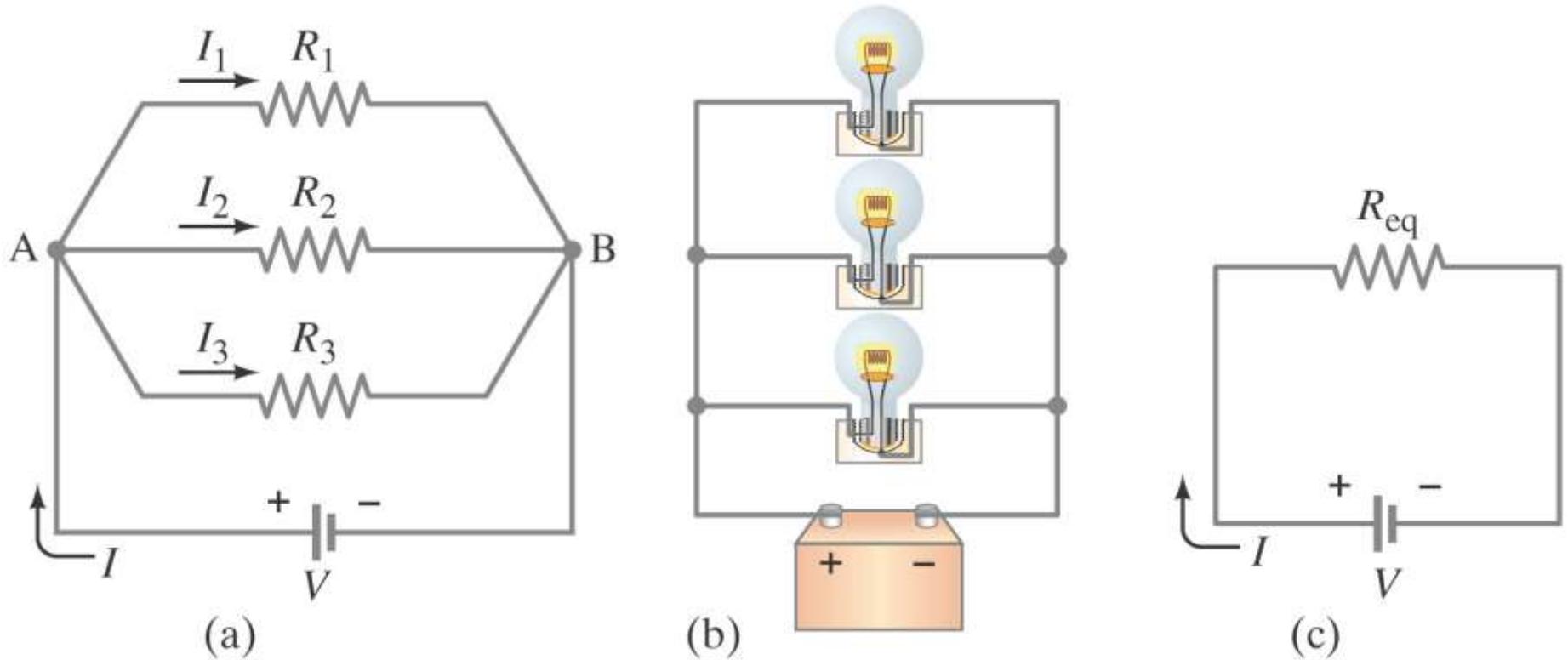
# 19.2 Resistors in Series and in Parallel

A parallel connection splits the current; the voltage across each resistor is the same:



## 19.2 Resistors in Series and in Parallel

The total current is the sum of the currents across each resistor:

$$I = I_1 + I_2 + I_3$$
$$\frac{V}{R_{\text{eq}}} = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$$


## 19.2 Resistors in Series and in Parallel

This gives the reciprocal of the equivalent resistance:

$$\frac{1}{R_{\text{eq}}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \quad (19-4)$$
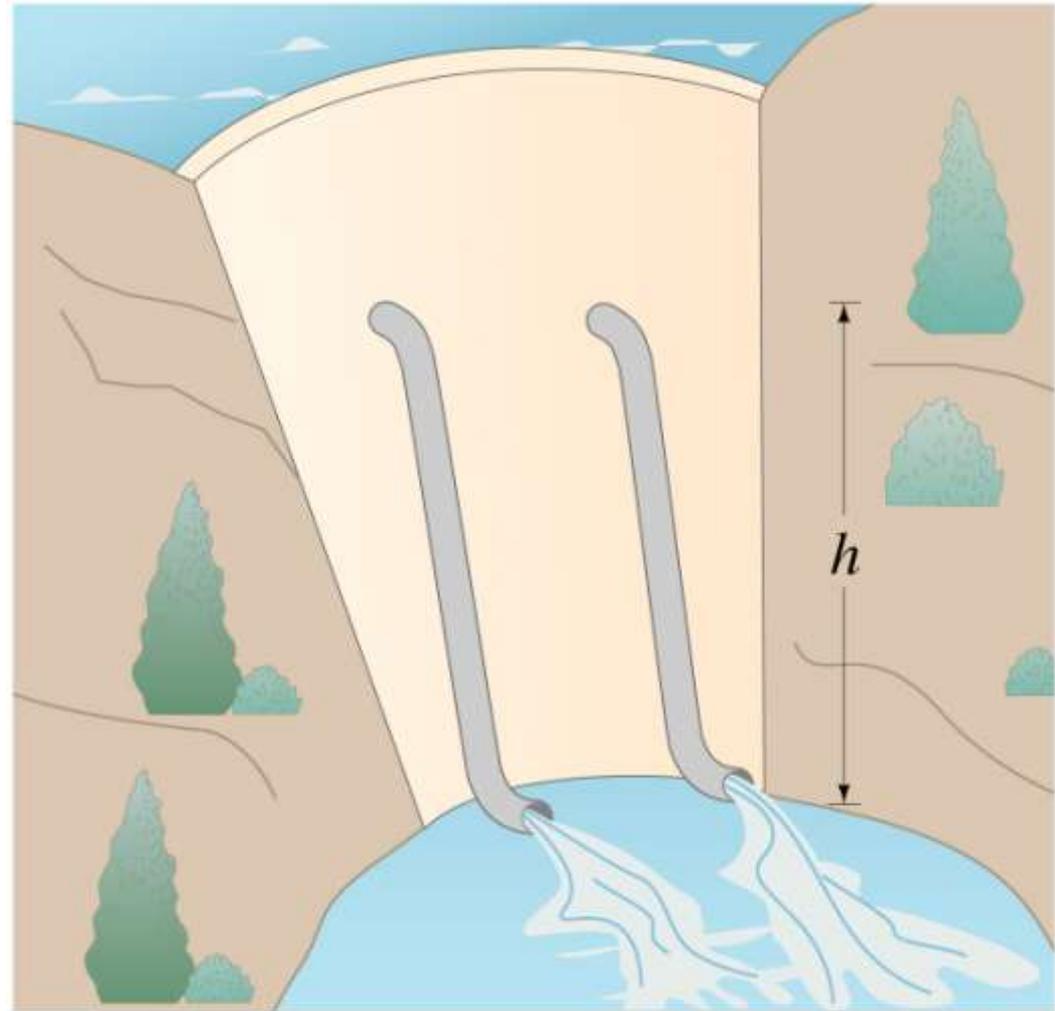
# 19.2 Resistors in Series and in Parallel

An analogy using water may be helpful in visualizing parallel circuits:




## 19.2 Resistors in Series and in Parallel



Time for a Gizmo!
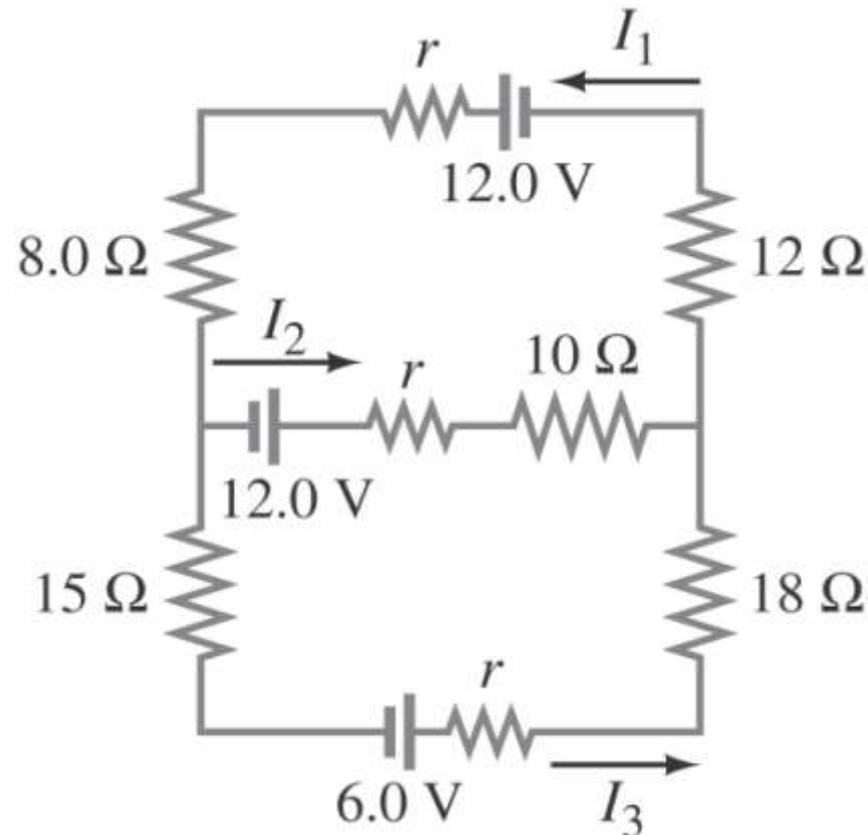
## 19.3 Kirchhoff's Rules


Some circuits cannot be broken down into series and parallel connections.


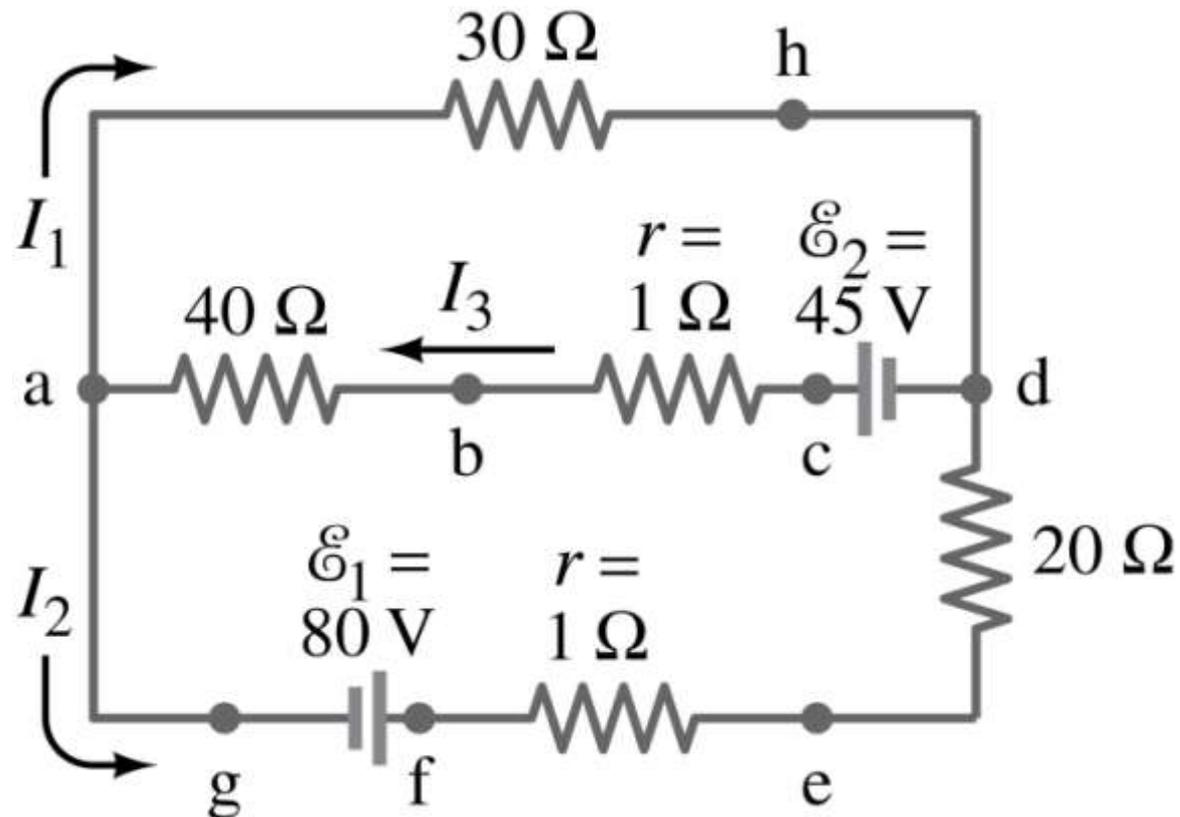
## 19.3 Kirchhoff's Rules



For these circuits we use Kirchhoff's rules.

**Junction rule:** The sum of currents entering a junction equals the sum of the currents leaving it.



# 19.3 Kirchhoff's Rules

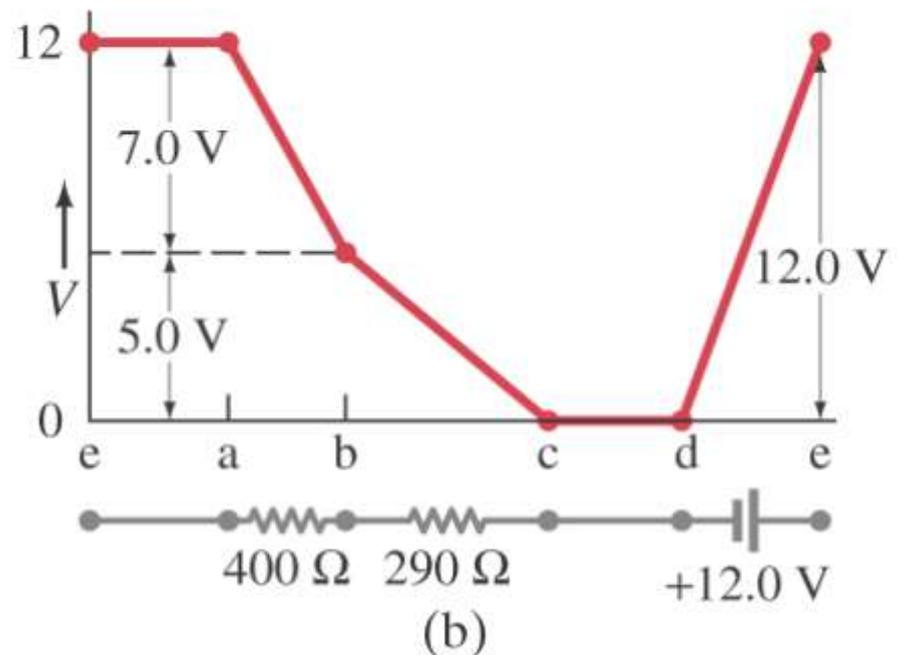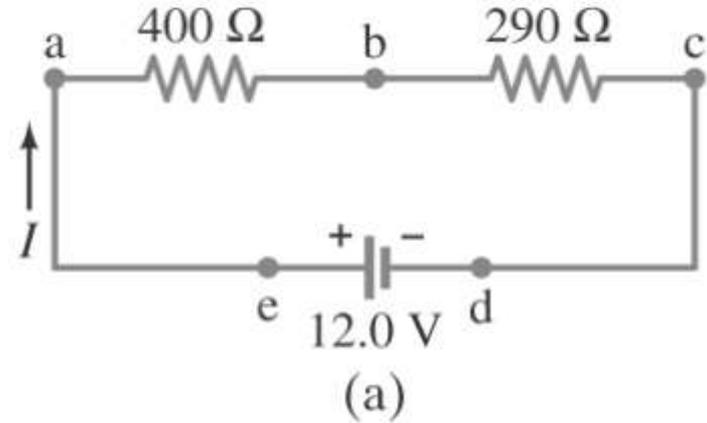**Loop rule: The sum of the changes in potential around a closed loop is zero.**




## 19.3 Kirchhoff's Rules

### Problem Solving: Kirchhoff's Rules

1. Label each current.
2. Identify unknowns.
3. Apply junction and loop rules; you will need as many independent equations as there are unknowns.
4. Solve the equations, being careful with signs.

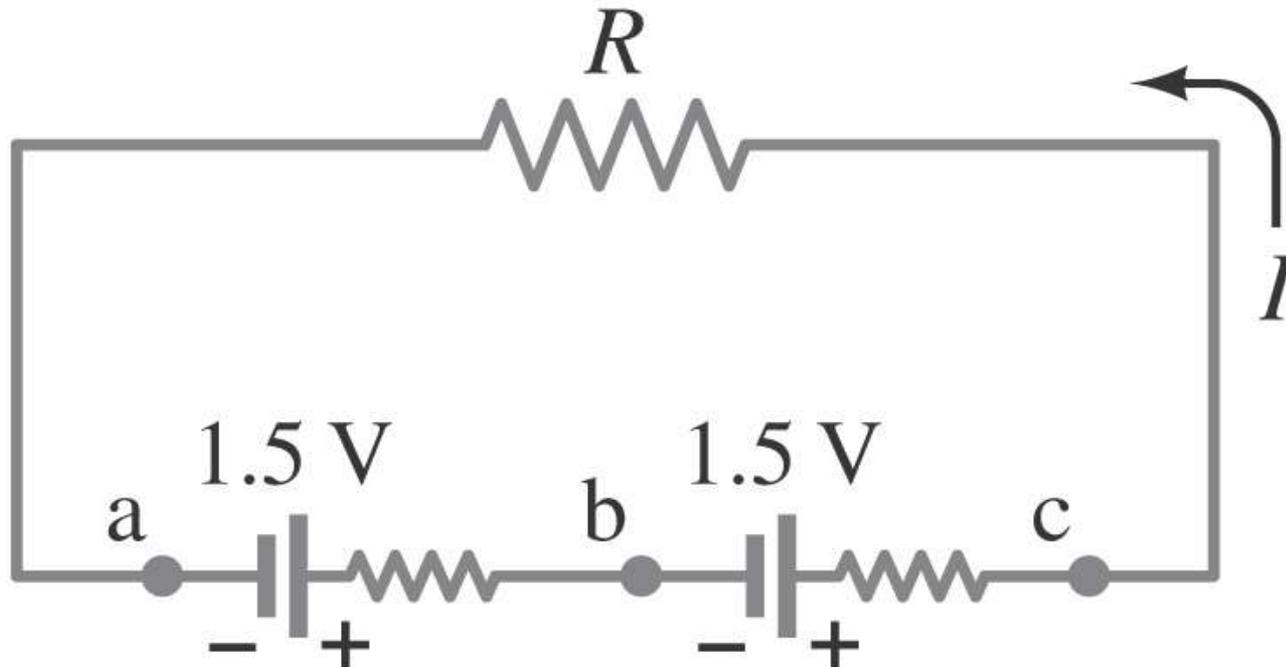
## 19.4 EMFs in Series and in Parallel; Charging a Battery

EMFs in series in the same direction: total voltage is the sum of the separate voltages



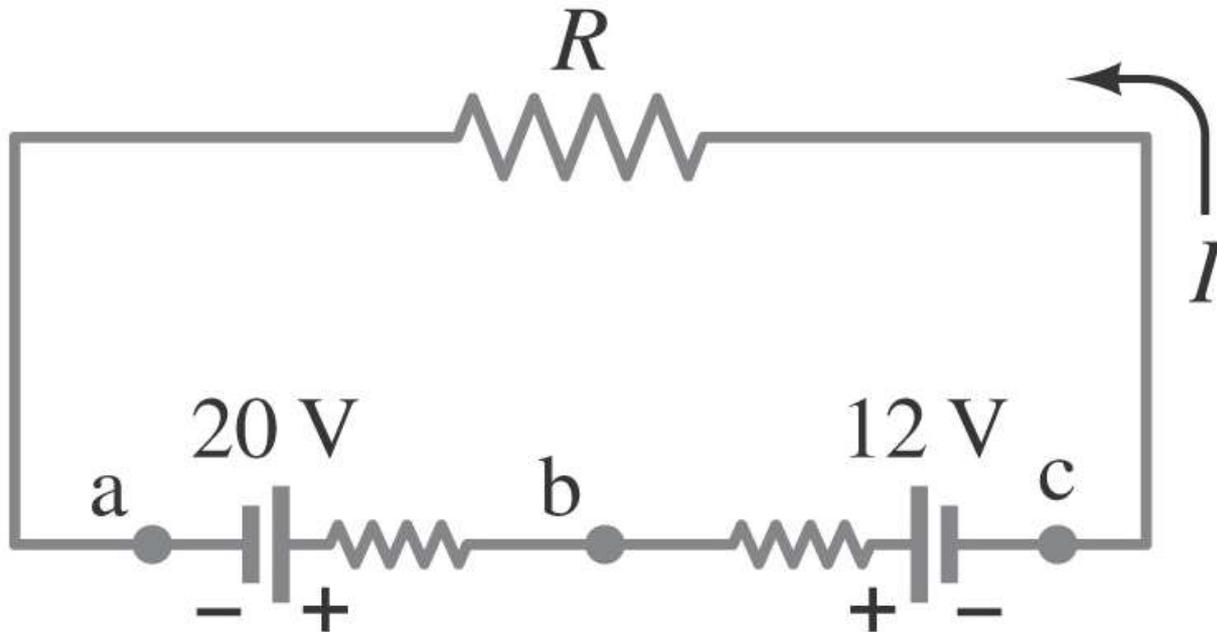
## 19.4 EMFs in Series and in Parallel; Charging a Battery

EMFs in series, opposite direction: total voltage is the difference, but the lower-voltage battery is charged.



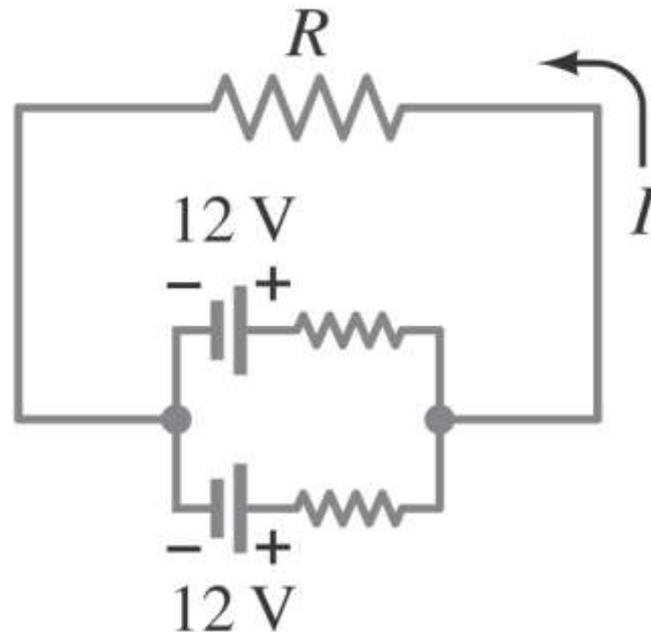
## 19.4 EMFs in Series and in Parallel; Charging a Battery

EMFs in parallel only make sense if the voltages are the same; this arrangement can produce more current than a single emf.


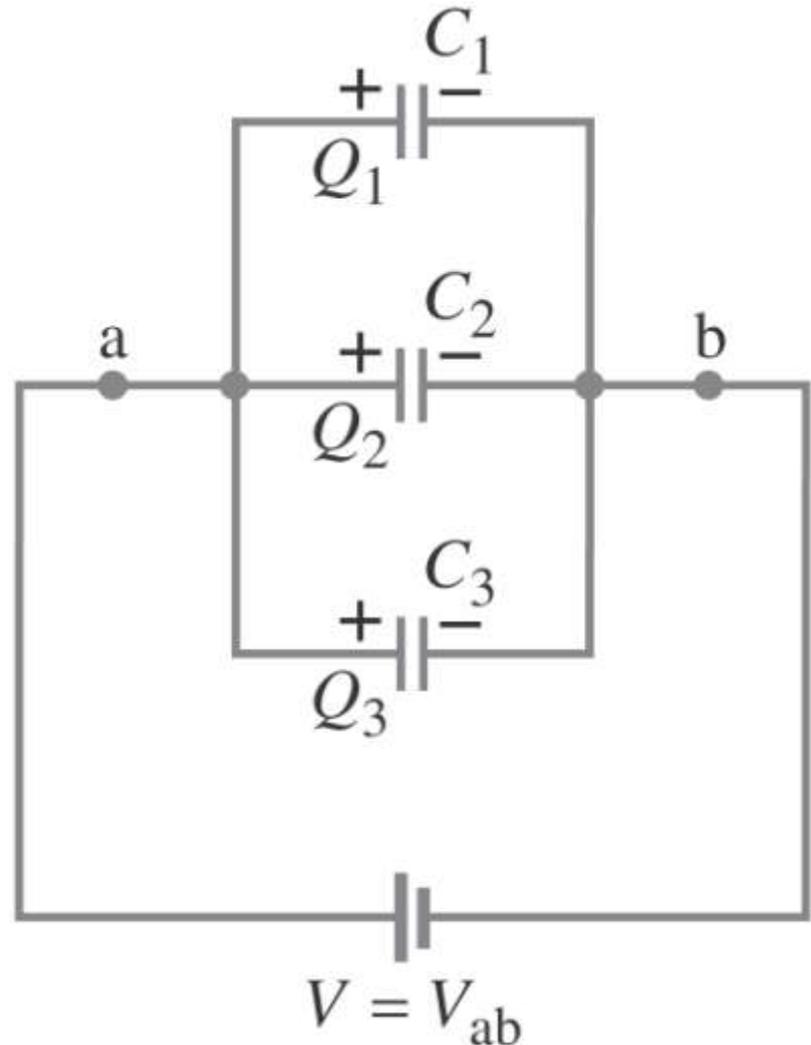
# 19.5 Circuits Containing Capacitors in Series and in Parallel

Capacitors in parallel have the same voltage across each one:



## 19.5 Circuits Containing Capacitors in Series and in Parallel


In this case, the total capacitance is the sum:

$$C_{\text{eq}} V = C_1 V + C_2 V + C_3 V = (C_1 + C_2 + C_3)V$$

$$C_{\text{eq}} = C_1 + C_2 + C_3 \quad (19-5)$$
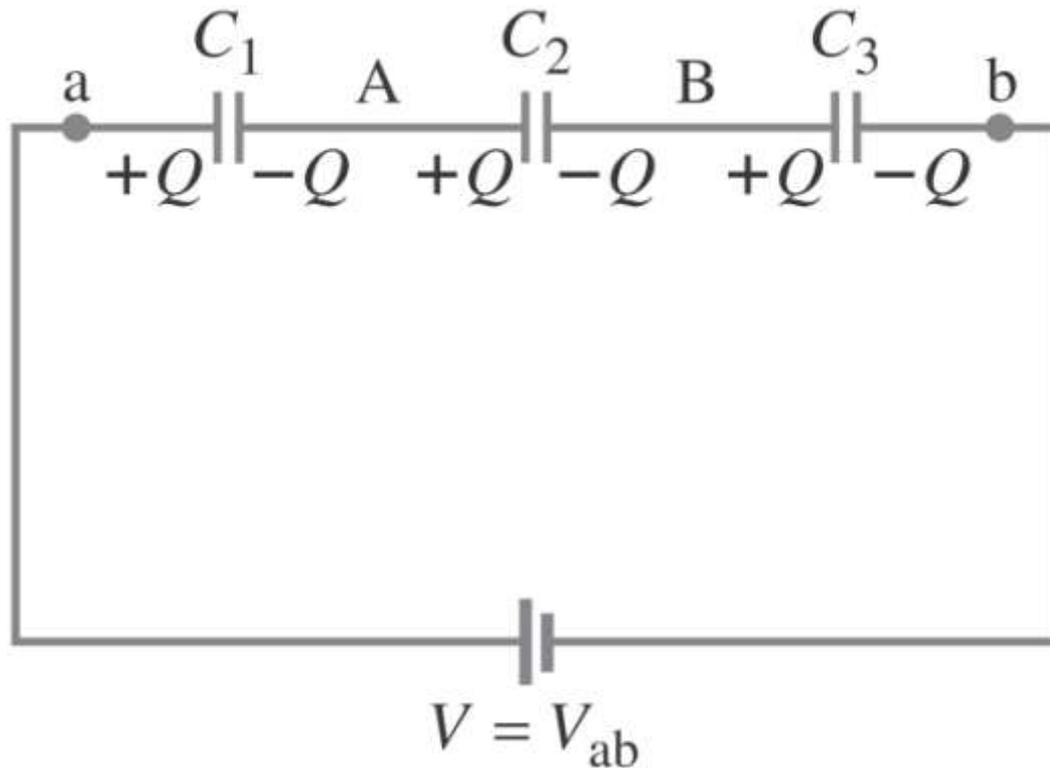
# 19.5 Circuits Containing Capacitors in Series and in Parallel

Capacitors in series have the same charge:



## 19.5 Circuits Containing Capacitors in Series and in Parallel


In this case, the reciprocals of the capacitances add to give the reciprocal of the equivalent capacitance:

$$\frac{Q}{C_{\text{eq}}} = \frac{Q}{C_1} + \frac{Q}{C_2} + \frac{Q}{C_3} = Q \left( \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \right)$$

$$\frac{1}{C_{\text{eq}}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \quad (19-6)$$
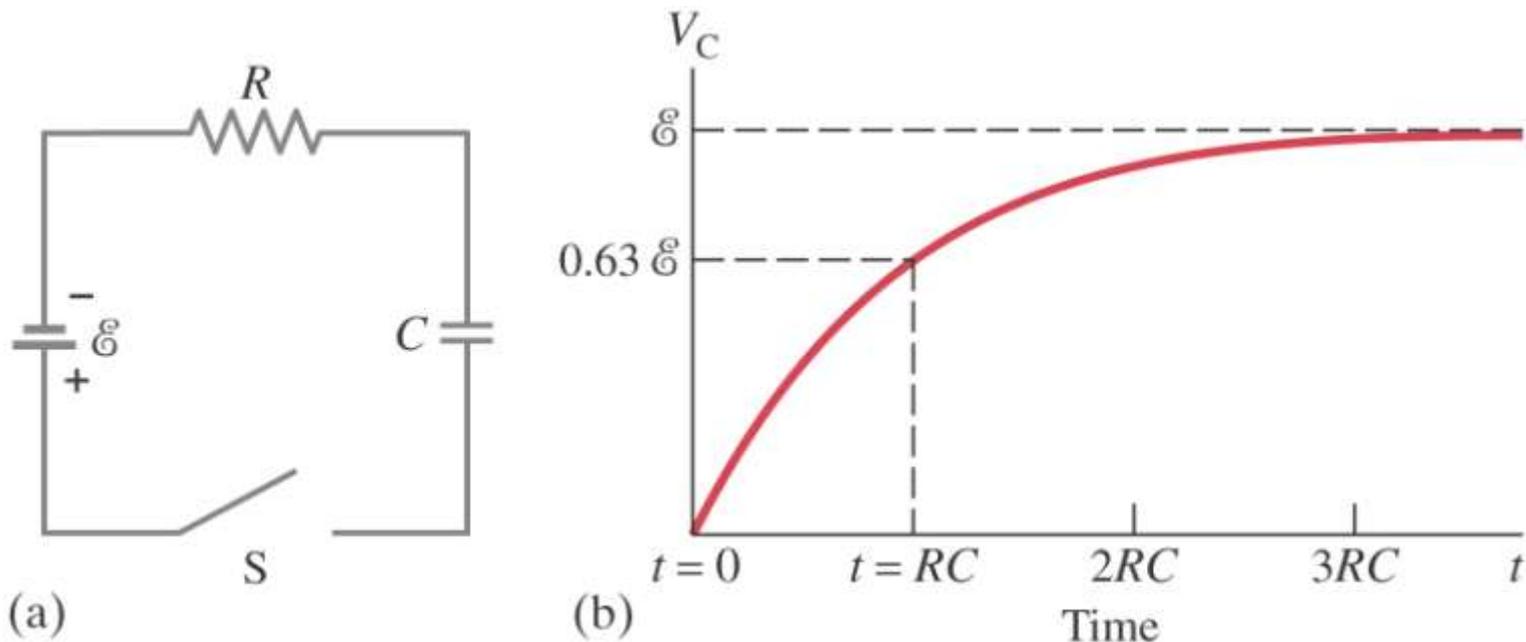
# 19.6 RC Circuits – Resistor and Capacitor in Series

When the switch is closed, the capacitor will begin to charge.



## 19.6 RC Circuits – Resistor and Capacitor in Series

The voltage across the capacitor increases with time:


$$V_C = \mathcal{E}(1 - e^{-t/RC})$$

This is a type of exponential.


# 19.6 RC Circuits – Resistor and Capacitor in Series

If an isolated charged capacitor is connected across a resistor, it discharges:

$$Q = Q_0 e^{-t/RC}$$

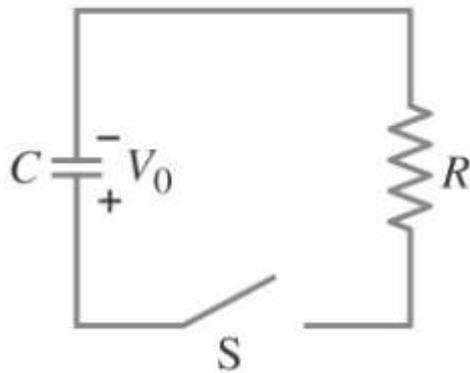

(a)

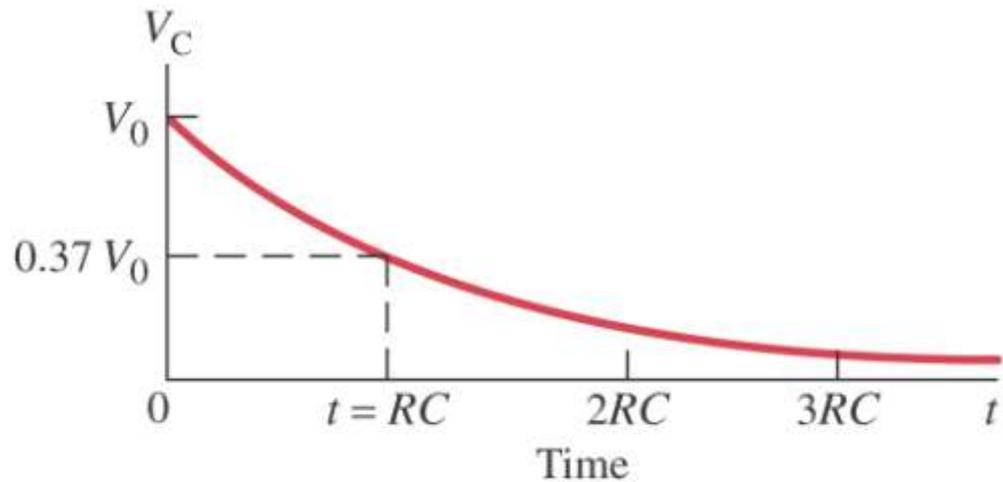

Time

(b)


## 19.7 Electric Hazards

**Even very small currents – 10 to 100 mA can be dangerous, disrupting the nervous system. Larger currents may also cause burns.**

**Household voltage can be lethal if you are wet and in good contact with the ground. Be careful!**

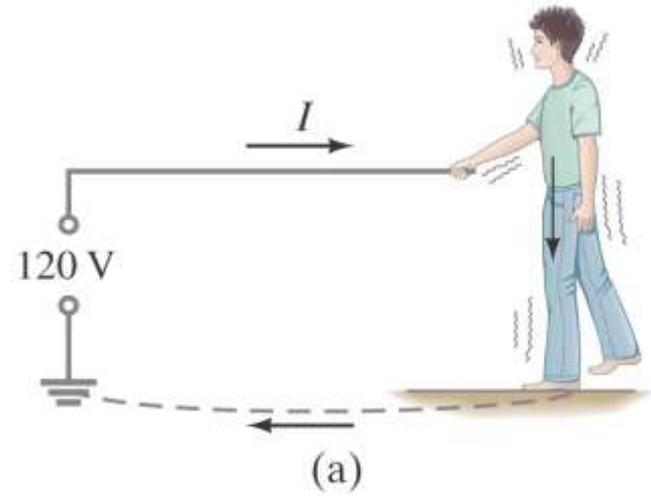
# 19.7 Electric Hazards

A person receiving a shock has become part of a complete circuit.



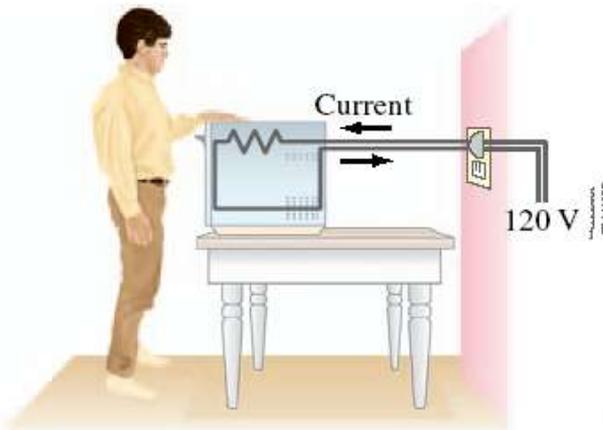
# 19.7 Electric Hazards


Faulty wiring and improper grounding can be hazardous. Make sure electrical work is done by a professional.



(a)

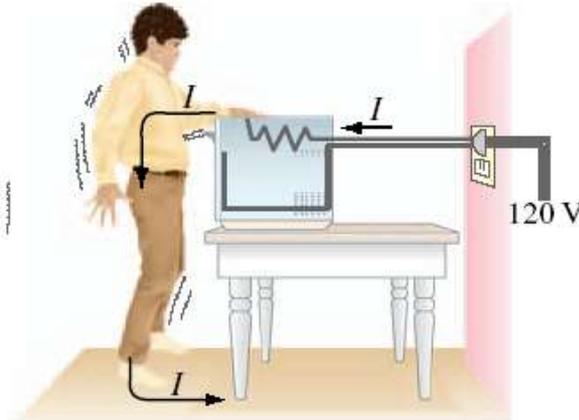

(b)

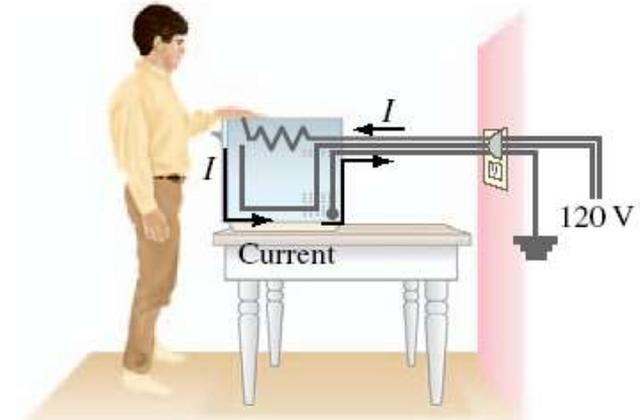


(c)
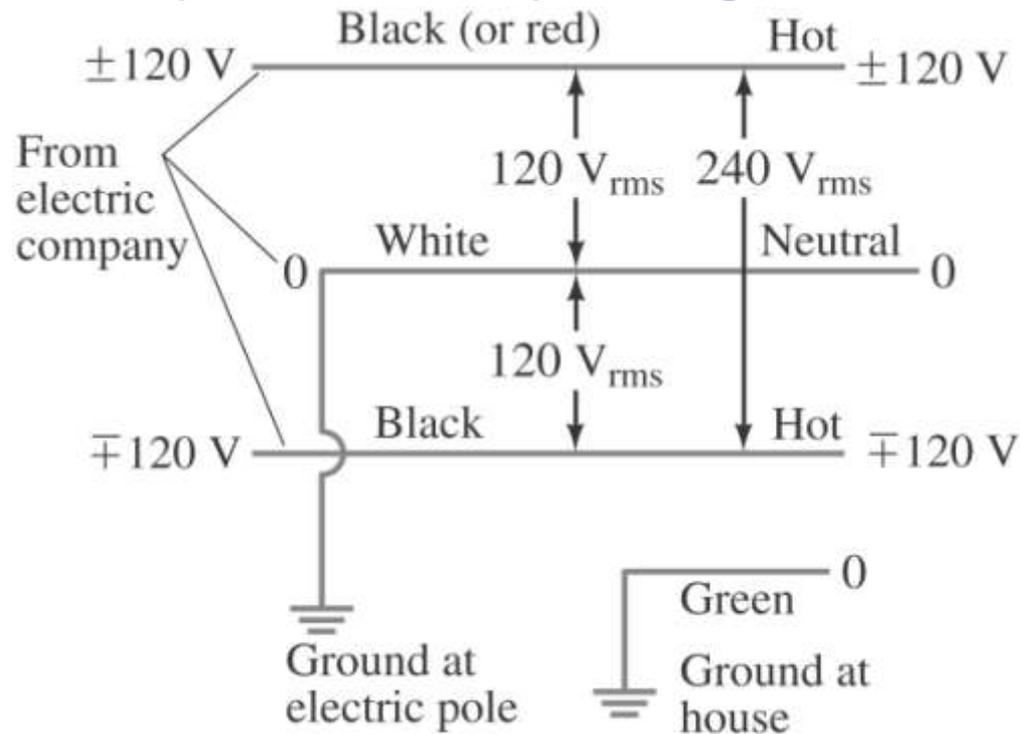
# 19.7 Electric Hazards

The safest plugs are those with three prongs; they have a separate ground line.


Here is an example of household wiring – colors can vary, though! Be sure you know which is the hot wire before you do anything.


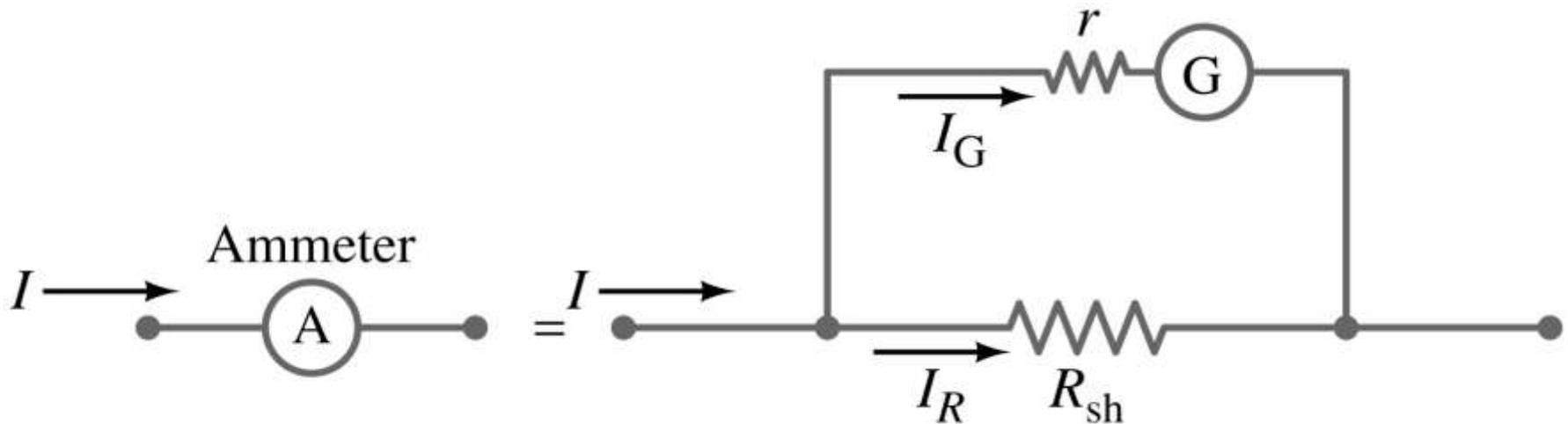
## 19.8 Ammeters and Voltmeters


An ammeter measures current; a voltmeter measures voltage. Both are based on galvanometers, unless they are digital.

The current in a circuit passes through the ammeter; the ammeter should have low resistance so as not to affect the current.


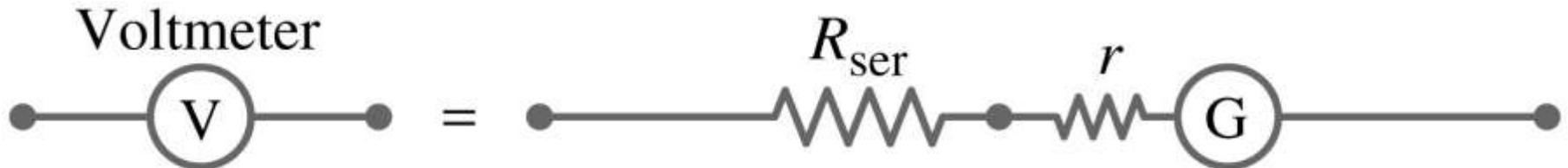
## 19.8 Ammeters and Voltmeters


A voltmeter should not affect the voltage across the circuit element it is measuring; therefore its resistance should be very large.



Copyright © 2005 Pearson Prentice Hall, Inc.

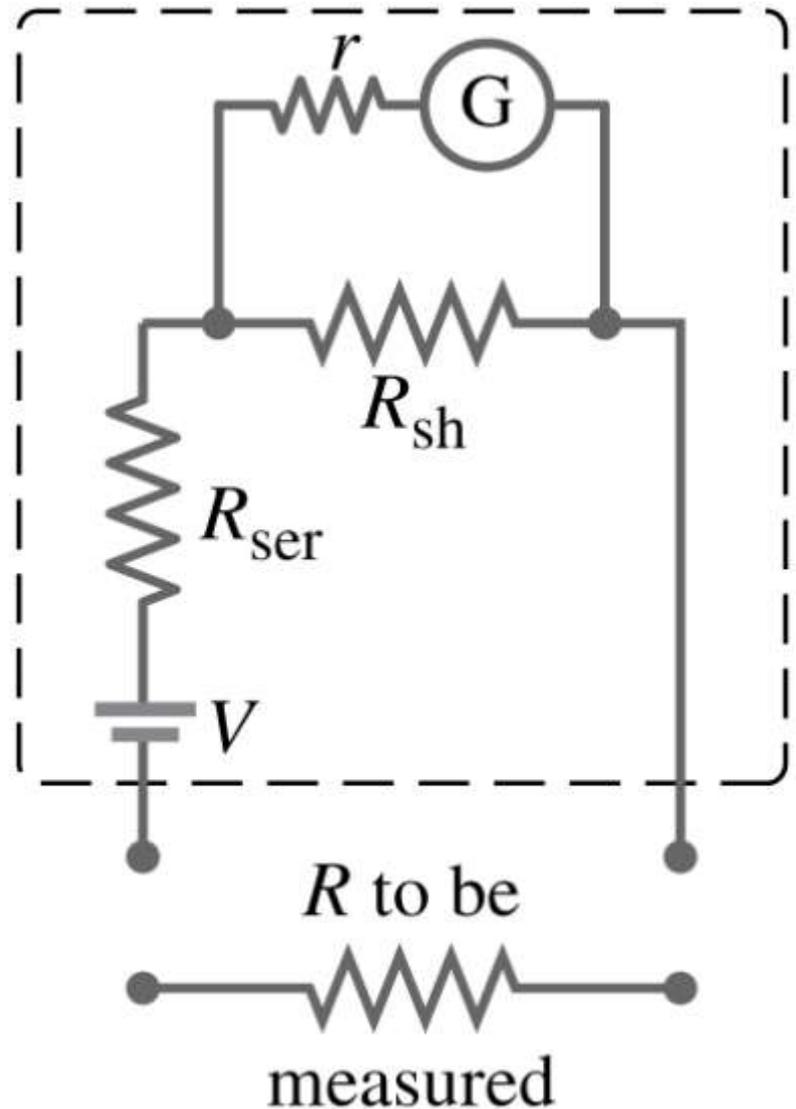
## 19.8 Ammeters and Voltmeters

An ohmmeter measures resistance; it requires a battery to provide a current



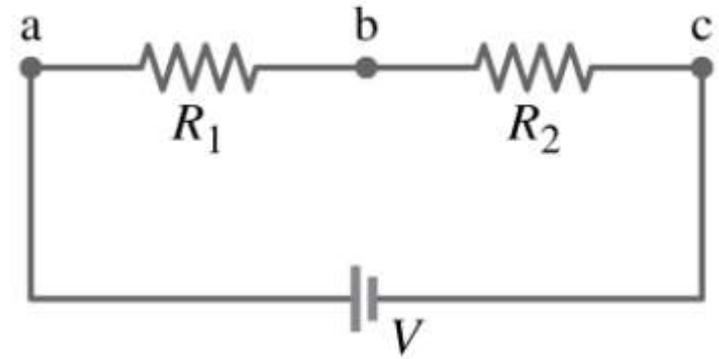
## 19.8 Ammeters and Voltmeters

If the meter has too much or (in this case) too little resistance, it can affect the measurement.



(a)

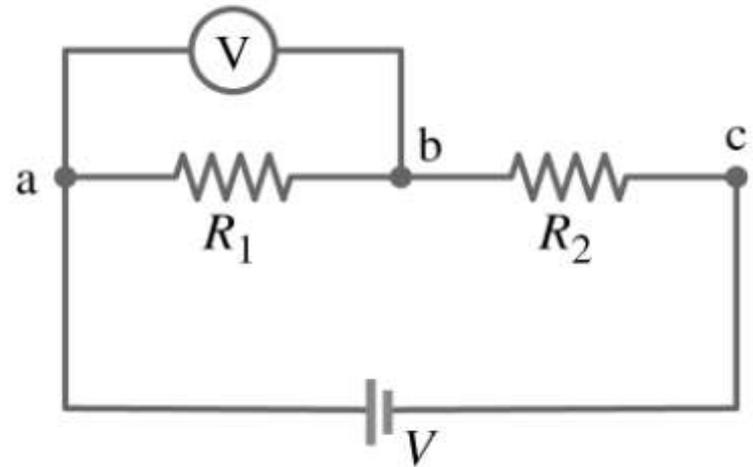

(b)

# Summary of Chapter 19

- A source of emf transforms energy from some other form to electrical energy
- A battery is a source of emf in parallel with an internal resistance
- Resistors in series:

$$R_{\text{eq}} = R_1 + R_2 + R_3$$

# Summary of Chapter 19

- **Resistors in parallel:**

$$\frac{1}{R_{\text{eq}}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

- **Kirchhoff's rules:**
  1. **sum of currents entering a junction equals sum of currents leaving it**
  2. **total potential difference around closed loop is zero**

# Summary of Chapter 19

- **Capacitors in parallel:**

$$C_{\text{eq}} = C_1 + C_2 + C_3$$

- **Capacitors in series:**

$$\frac{1}{C_{\text{eq}}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

# Summary of Chapter 19

- **RC circuit has a characteristic time constant:**

$$\tau = RC$$

- **To avoid shocks, don't allow your body to become part of a complete circuit**
- **Ammeter: measures current**
- **Voltmeter: measures voltage**